

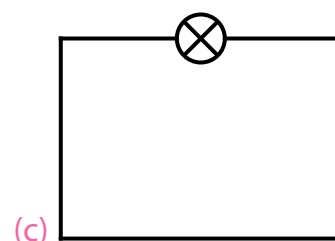
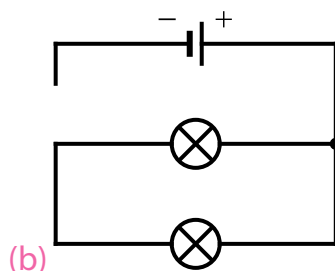
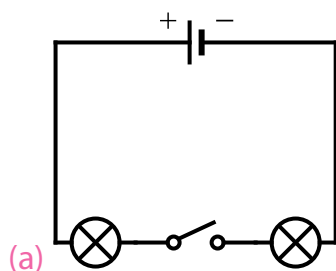
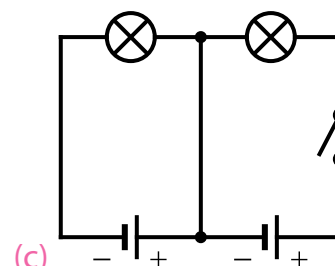


- 1 Which of these four situations are open circuits and which are closed circuits?
- (a) The kettle is off.
- (b) The power button on the remote control is being pressed.
- (c) A remote controlled plane that is flying.
- (d) A washing machine that is turned off.



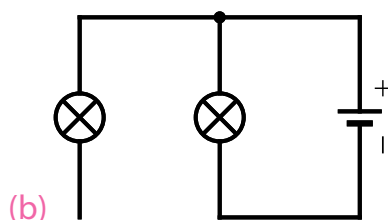
- 2 Which of these circuits are open and which are closed?





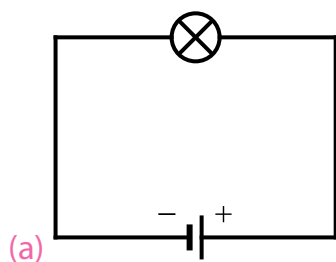
- 3 Draw around the closed loop in these circuits.



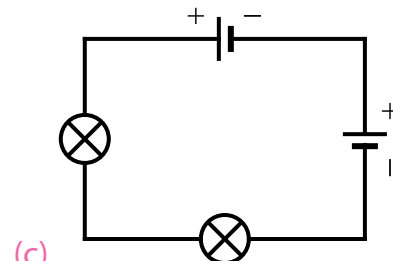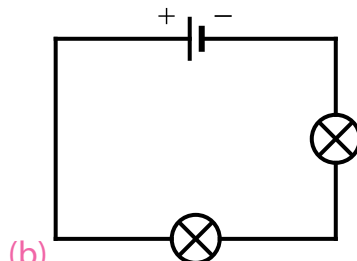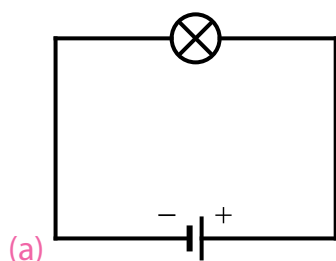
- 4 Draw arrows on the circuits in the direction of the current.



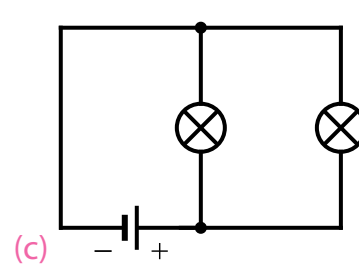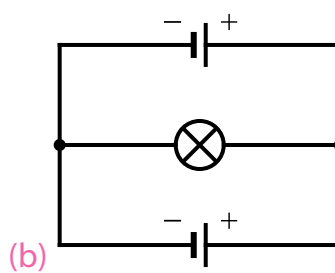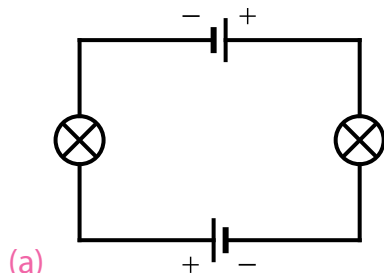
- 5 Draw arrows on the circuits in the direction of the current.



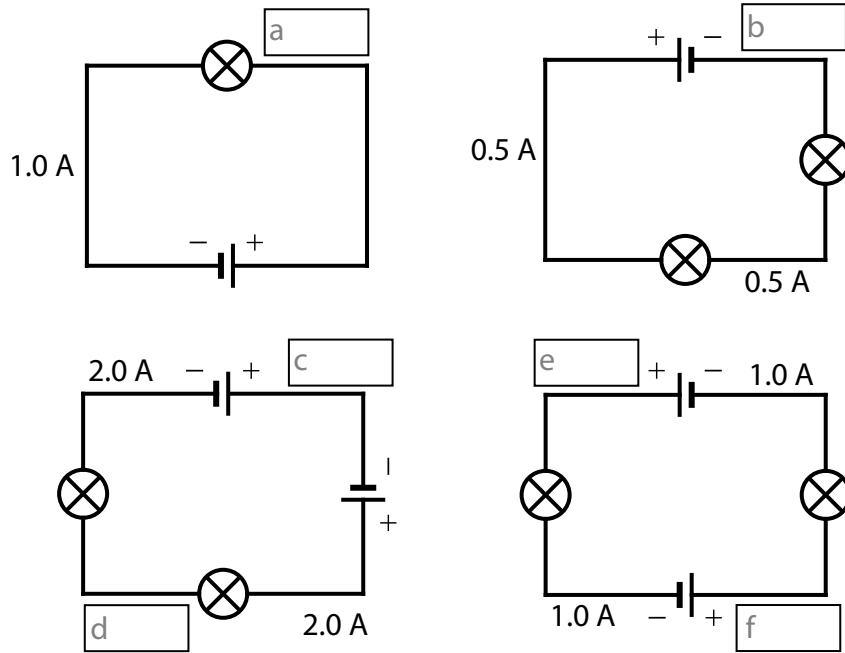
6 Write down the current in each of the boxes.



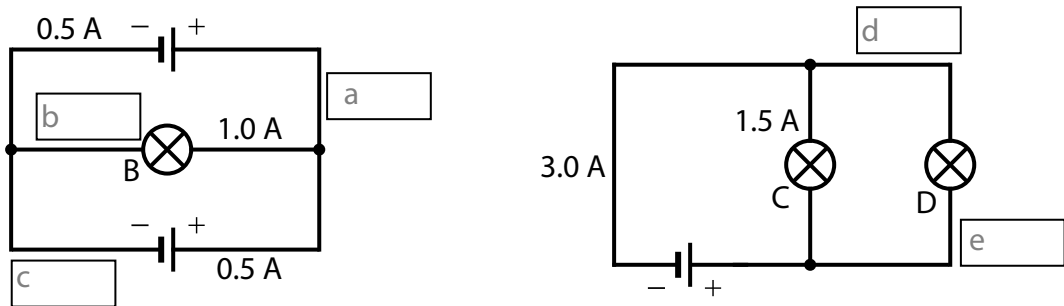7 Write down the current in each of the boxes.



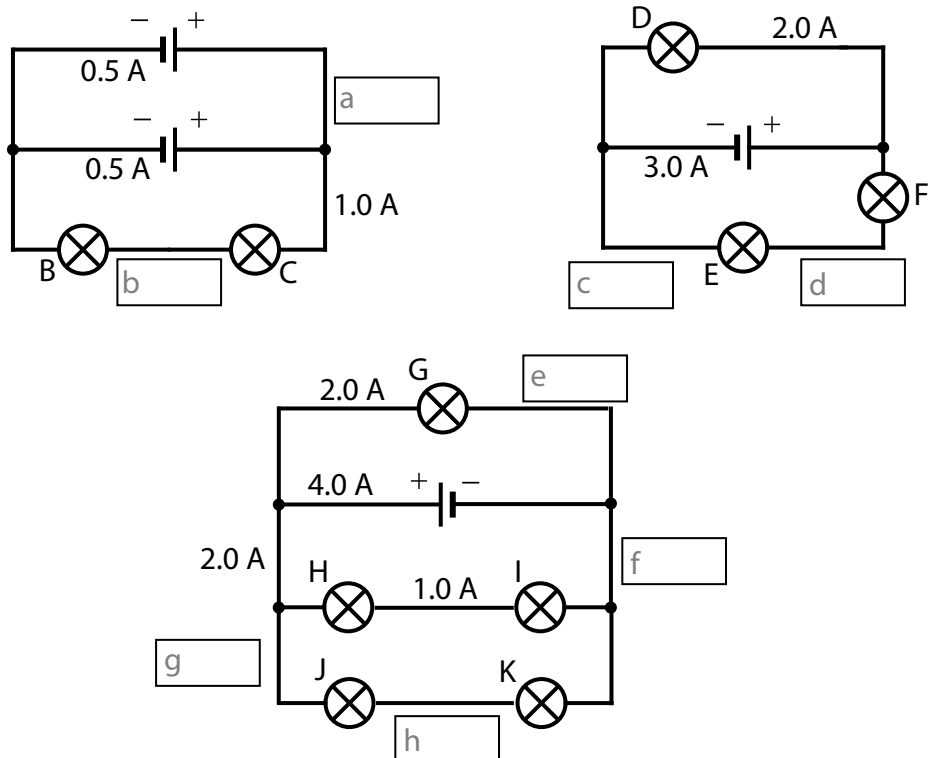8 Write down the current in each of the boxes.




- 9 Go back to the circuits in questions 7 and 8. Which light bulbs are in **series** and which are in **parallel** with the other bulbs in the circuits.

- 10 Fill in the sentences with the words **brighter, current, light up, more**.

A light bulb will _____ if there is a _____ passing through it. The _____ current passes through a light bulb, the _____ the light bulb will shine.

- 11 Go back to the circuits in questions 7 and 8. The light bulbs are identical in those circuits. Which light bulbs will have the **same brightness**, which will be the **brightest** and which will be the **dimnest** in each circuit?

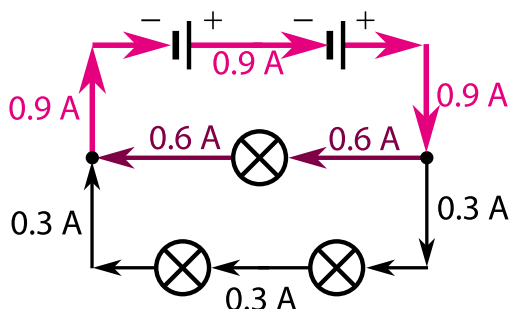- 12 What have you noticed about current and light bulbs while working through these questions? Fill in the sentences with the words **series, parallel, shared, same, dimmest**.



(a) The current through two light bulbs in **series** will be the _____. They will have the _____ brightness, if they are identical.

(b) The current through light bulbs in **parallel** will be _____. The branch with the least amount of current will have the _____ light bulbs.

- 13 Label which light bulbs will have the **same brightness**, which will be the **brightest** and which will be the **dimnest** within each circuit.

