



[https://isaacscience.org/question\\_decks#ipts25\\_sat\\_4b\\_r1](https://isaacscience.org/question_decks#ipts25_sat_4b_r1)

# Electricity ‘under the hood’

Anton Machacek, Associate Director

This symposium is  
generously funded  
by



**making  
physics  
matter**

# Visualizing Potential and Current



- What pictures and models do we use to help?
- For a particular model or picture
  - What does it do well?
  - What does it do badly?
  - Where have we used it to good effect?
- What about not using a model at all?

This symposium is  
generously funded  
by



**making  
physics  
matter**

# Potential and Current – analogies/models





Potential	Current
Height (roller coaster)	Trains each hour
Pressure (hydraulic fluid in pipe)	Flow rate of fluid (volume per unit time)
Temperature (of point in thermal system)	Heat flow rate (energy per unit time)

This symposium is  
generously funded  
by




**making  
physics  
matter**

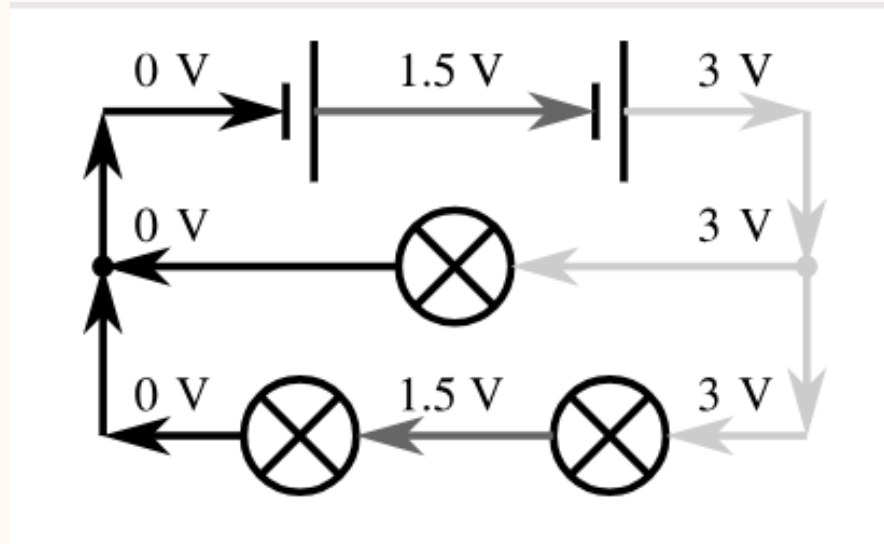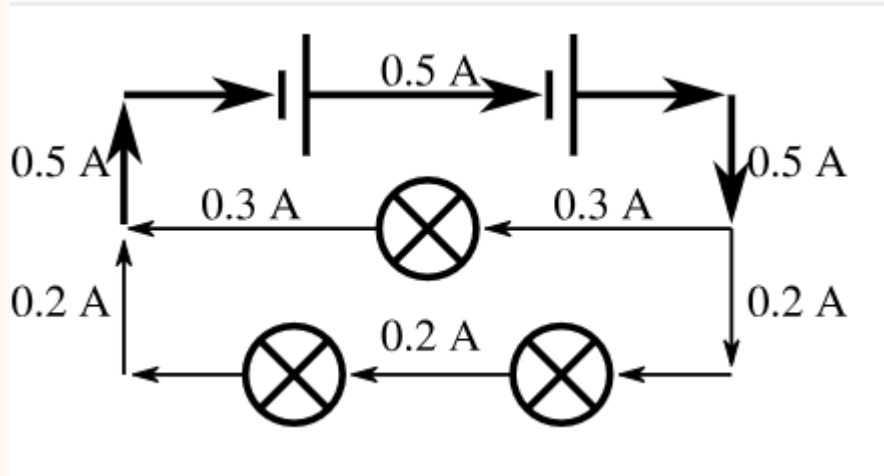
# Circuit Rules (easier than the Highway Code?)



- What makes this circuit hard?

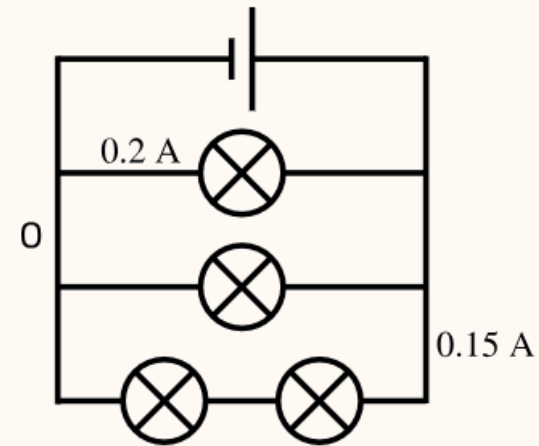

- And this one?



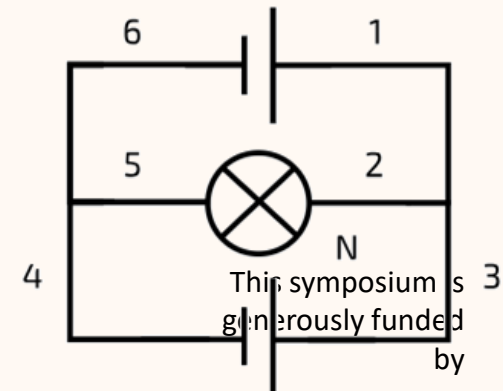


making  
physics  
matter

# Solving circuits 1



- Combine then separate resistances

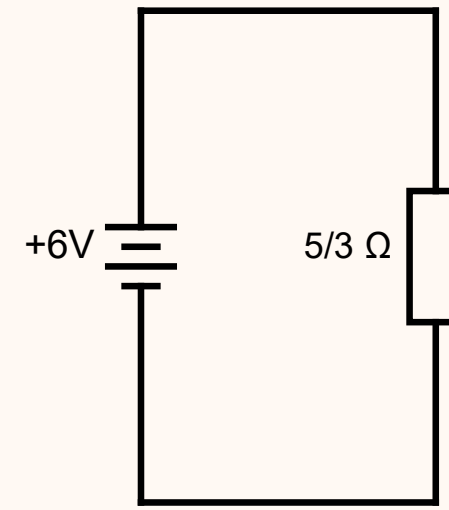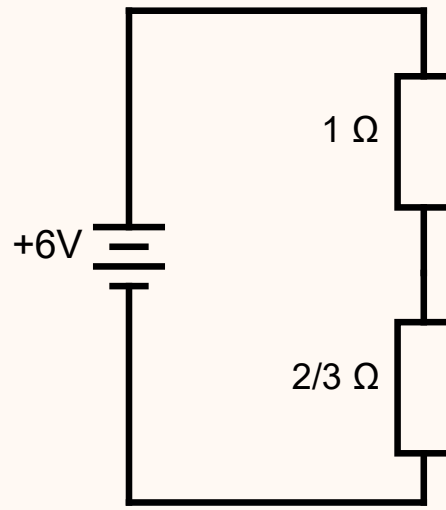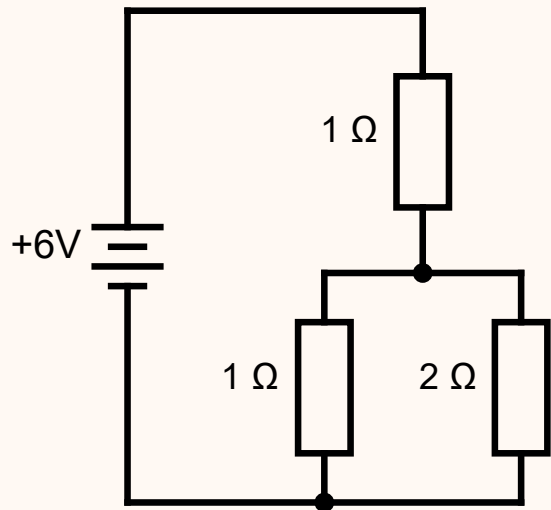

This symposium is  
generously funded  
by




**making  
physics  
matter**

# Solving circuits 2



- Raw algebra

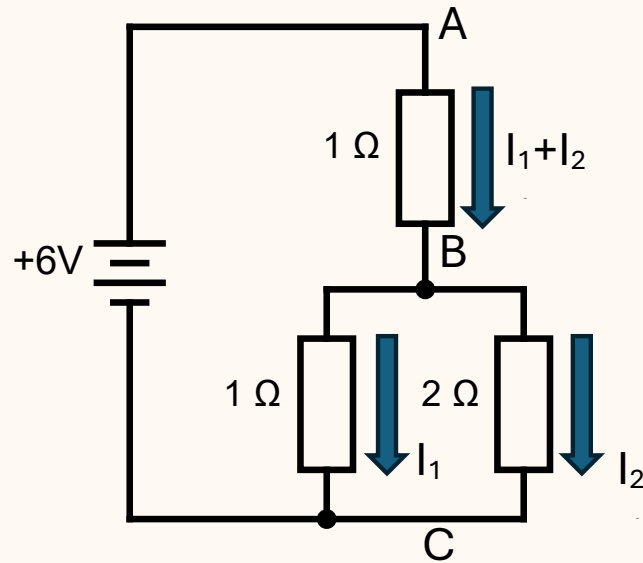

This symposium is  
generously funded  
by




**making  
physics  
matter**

# Solving circuits 3



- Loop currents

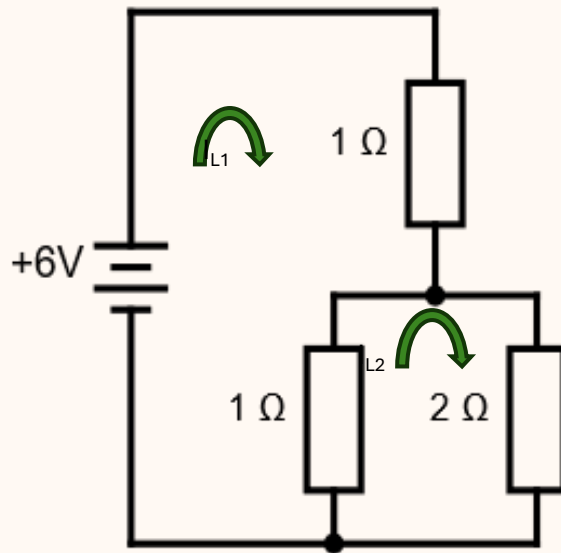

From O, clockwise

$$6 - 1 \times I_{L1} - 1 \times (I_{L1} - I_{L2}) = 0$$

$$-1 \times (I_{L2} - I_{L1}) - 2 \times I_{L2} = 0$$

This symposium is  
generously funded  
by





**making  
physics  
matter**
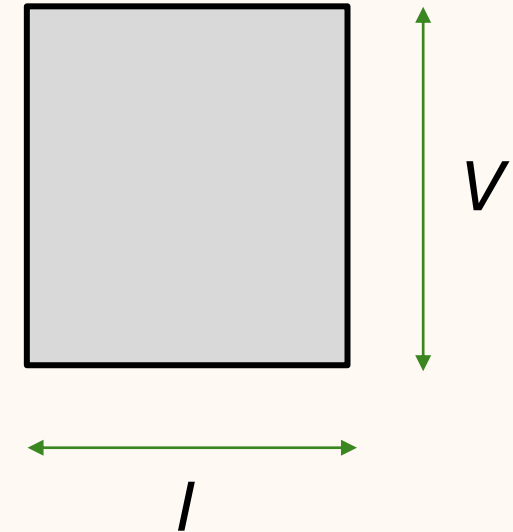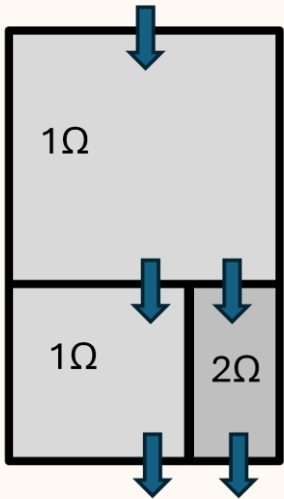
# Solving circuits 4



- AVOW diagram: components are rectangles
  - Area is...
  - Gradient of diagonal is...
  - Circuit laws mean...



This symposium is  
generously funded  
by




**making  
physics  
matter**



# Solve circuits 5



- Matrix

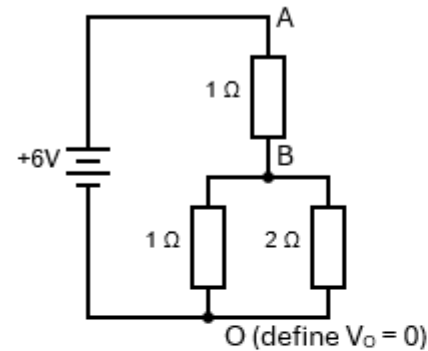

$$I_A = I_{AB}$$

$$I_A = G_{AB} (V_A - V_B) = 1 \times (V_A - V_B)$$

$$I_B = I_{BA} + I_{BO}$$

$$0 = G_{BA} (V_B - V_A) + G_{BO} (V_B - V_O)$$

$$0 = 1 \times (V_B - V_A) + (3/2) \times V_B$$

$$\begin{pmatrix} I_A \\ 0 \end{pmatrix} = \begin{pmatrix} 1 & -1 \\ -1 & 5/2 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} \text{ so } \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \frac{1}{3/2} \begin{pmatrix} 5/2 & 1 \\ 1 & 1 \end{pmatrix} \begin{pmatrix} I_A \\ 0 \end{pmatrix}$$

In general: (this matrix for 4 points O, A, B, C)

$$\begin{pmatrix} I_A \\ I_B \\ I_C \end{pmatrix} = \begin{pmatrix} G_{AB} + G_{AC} + G_{AO} & -G_{AB} & -G_{AC} \\ -G_{AB} & G_{BA} + G_{BC} + G_{BO} & -G_{BC} \\ -G_{AC} & -G_{BC} & G_{CA} + G_{CB} + G_{CO} \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix}$$

This symposium is  
generously funded  
by



**making  
physics  
matter**

# Ohm's law unpacked



- Assume:
  - Free electrons in a metal accelerate as a result of the potential difference provided by the battery.
  - They stop as a result of a collision, and re-accelerate in a repeating cycle.
  - The average time between collisions is called the **relaxation time**.
- [https://isaacscience.org/questions/ohms\\_law\\_unpacked](https://isaacscience.org/questions/ohms_law_unpacked)

# Electron speed – exclusion principle



- The electron is a fermion. So what?
- We can use ideas of standing waves to work out the speed of the colliding electrons:
  - [https://isaacscience.org/questions/fermi\\_velocity](https://isaacscience.org/questions/fermi_velocity)