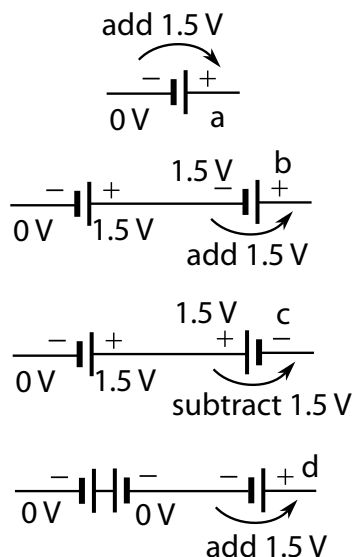


## Potential and Circuits Practice

- 1 Cells are linked together in different ways. What is the total potential energy for each combination?




(a) What is the potential at (a)?

(b) Two cells are connected together. The potential at the negative terminal of cell 2 is 1.5 V. What is the potential at (b)?


(c) The second cell is connected in reverse. What is the potential at (c)?

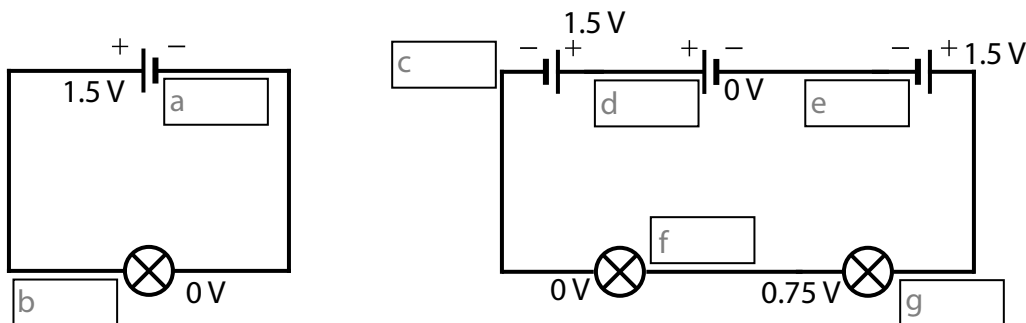(d) A third cell is now connected. What is the potential at (d)?



- 2 Write down the potential in each of the boxes.



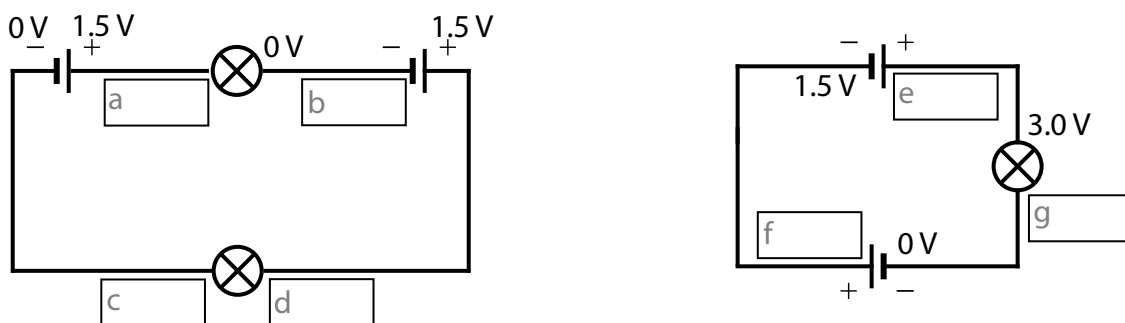
- 3 Write down the potential in each of the boxes.



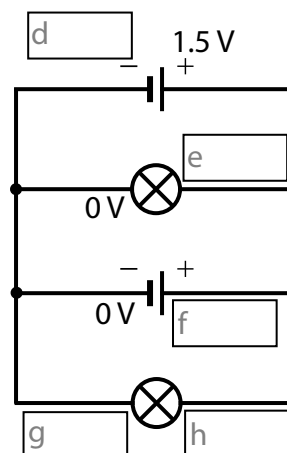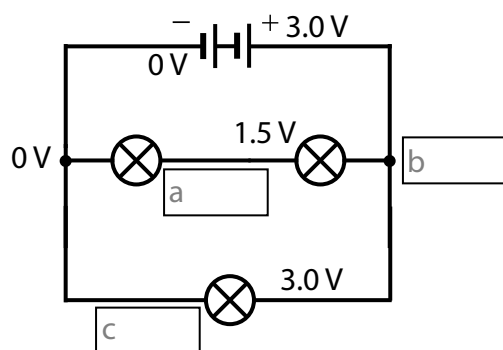4 Write down the potential in each of the boxes.




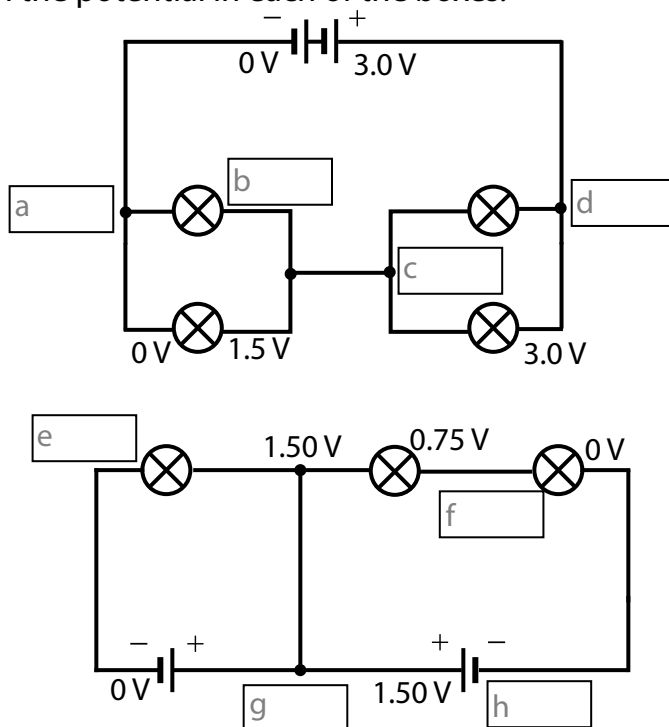5 Write down the potential in each of the boxes.



6 What is the potential difference for each cell combination or battery? Each cell has a potential difference of 1.5 V.

(a) 1-cell battery

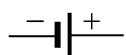

(b) 2-cell battery




(c) odd 3-cell battery



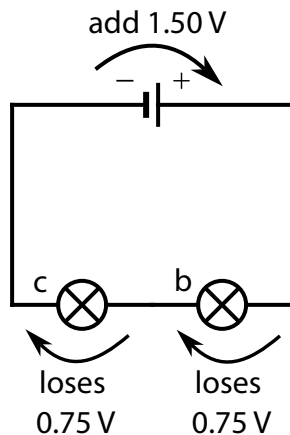(d) odd 4-cell battery




- 7 Complete the sentences with the words **series**, **parallel**, **branch**, **branches**, **next**, **shared**, **same**, **different**, **potential difference**.



(a) If two bulbs are \_\_\_\_\_ to each other on the same \_\_\_\_\_ of the circuit, we say they are in \_\_\_\_\_. The \_\_\_\_\_ is \_\_\_\_\_ across the two.

(b) What is the potential at (b)?

(c) What is the potential at (c)?

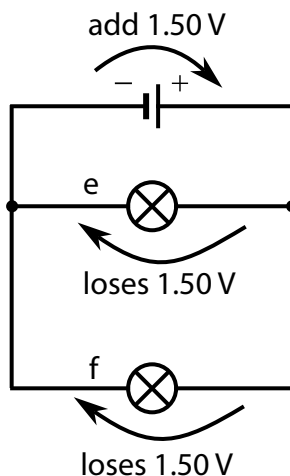

(d) If two bulbs are on \_\_\_\_\_ branches of the circuit, we say the bulbs are in \_\_\_\_\_. The \_\_\_\_\_ is \_\_\_\_\_ across the two \_\_\_\_\_ of the circuit.

(e) What is the potential at (e)?

(f) What is the potential at (f)?

- 8 Which bulbs in the circuits in question 4 are in series and which are in parallel?

- 9 Go back to the circuits in questions 2, 3, 4 and 5. What is the brightness of each bulb? Are they **normal**, **dimmer** or **brighter**?

- 10 A toy car needs 9.0 V to work.

(a) How many 1.5 V batteries will you need to make the car work? A 1.5 V battery means the potential difference across it is 1.5 V.

(b) Will you lay the batteries in the same direction in the car or in opposite directions?