



Physics. *You work it out.*

[Home](#) [Gameboard](#) [Physics](#) [Electricity](#) [Components](#) [Potential Dividers With LEDs 8.1](#)

Potential Dividers With LEDs 8.1

A Level

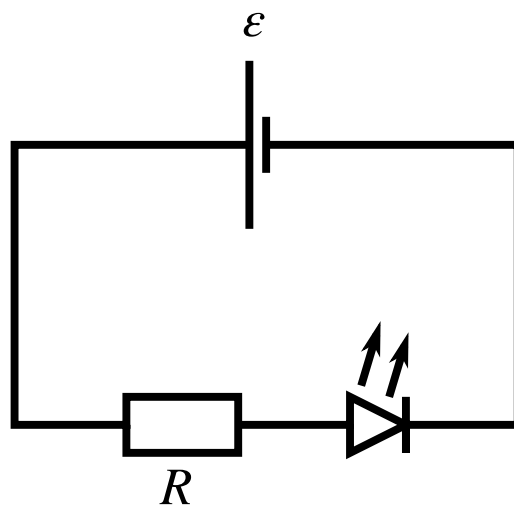


Figure 1: A circuit with a single cell in series with a resistor and an LED.

Quantities:

ε e.m.f. (V)

V p.d. across fixed resistor (V)

V_{LED} p.d. across LED (V)

I current through circuit (A)

R fixed resistor resistance (Ω)

E photon energy (J)

λ wavelength of emitted light (m)

Equations:

$$V = IR \quad \varepsilon = V_{\text{LED}} + V \quad V_{\text{LED}} = \frac{E}{e} \quad E = \frac{hc}{\lambda}$$

Use the equations above to derive expressions for:

Part A The resistance of the fixed resistor R

the resistance of the fixed resistor R in terms of the e.m.f. ε , the p.d. across the LED V_{LED} and the current I .

The following symbols may be useful: I , R , V_{LED} , ε

Part B The resistance of the fixed resistor R , using λ

the resistance of the fixed resistor R in terms of the e.m.f. ε , the wavelength of the LED λ , the current I and the physical constants h , c and e .

The following symbols may be useful: I , R , c , e , ε , h , λ

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.



Physics. *You work it out.*

[Home](#) [Gameboard](#) [Physics](#) [Electricity](#) [Components](#) [Potential Dividers With LEDs 8.3](#)

Potential Dividers With LEDs 8.3

A Level



A blue LED produces light of wavelength 480 nm. It is powered using a 9.00 V battery using the circuit design shown below. Assume that there is no internal resistance in the power supply.

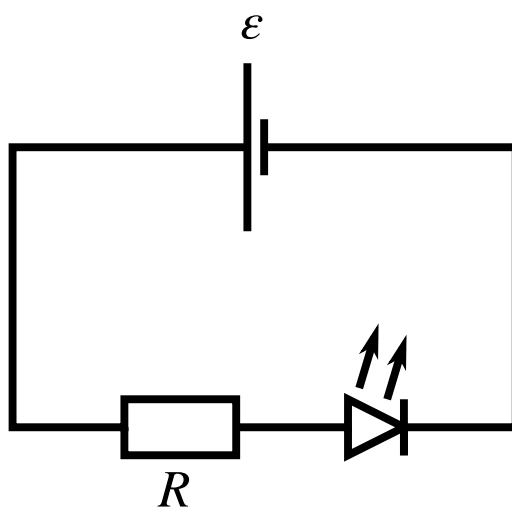


Figure 1: A circuit with a single cell in series with a resistor and an LED.

Part A The p.d. across the LED

Calculate the p.d. across the LED.

Part B The minimum value of R

Calculate the minimum value of R to ensure the current through the LED does not exceed 50.0 mA.

Part C The resistance of the LED

Calculate the resistance of the LED.

Gameboard:

STEM SMART Physics 30 - Complicated circuits

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.



Current Division 9.2

A Level

P

P

P

A $9.0\ \Omega$ resistor is connected in parallel with a $81\ \Omega$ resistor. What fraction of the total current flows through the $81\ \Omega$ resistor?

Gameboard:

[STEM SMART Physics 30 - Complicated circuits](#)

All materials on this site are licensed under the [Creative Commons license](#), unless stated otherwise.



Physics. *You work it out.*

[Home](#) [Gameboard](#) [Physics](#) [Electricity](#) [Resistors](#) [Current Division 9.4](#)

Current Division 9.4

A Level



I am going to connect two resistors in parallel to share a 13 A current so that 5.0 A flows through one resistor. The resistor with the larger resistance is a $2.2\ \Omega$ resistor. Calculate the resistance of the other resistor.

Gameboard:

STEM SMART Physics 30 - Complicated circuits

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.




Power in a Potential Divider 10.2



Calculate the load power P for an emf $\varepsilon = 240\text{ V}$ generator with internal resistance $2.5\ \Omega$ when it is supplying 4.2 A .

Gameboard:
[STEM SMART Physics 30 - Complicated circuits](#)

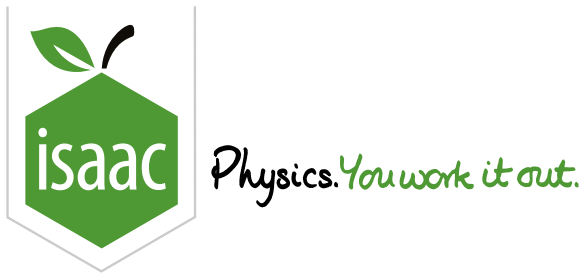All materials on this site are licensed under the [Creative Commons license](#), unless stated otherwise.



Power in a Potential Divider 10.8

A Level

P

P

P

A $\mathcal{E} = 5.4\text{ V}$ power supply (with $r = 8.0\text{ }\Omega$) powers a $50\text{ }\Omega$ phone. A voltmeter (with resistance $200\text{ }\Omega$) is connected to measure V .

Part A

Voltage V

How much voltage V is measured across the phone?


Part B

Power delivered

Calculate the power delivered to the phone.

Gameboard:
[STEM SMART Physics 30 - Complicated circuits](#)

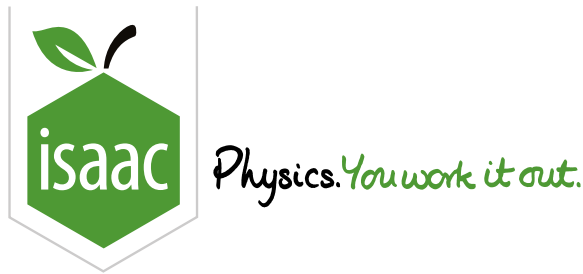All materials on this site are licensed under the [Creative Commons license](#), unless stated otherwise.



Non-linear I-V

GCSE

A Level

The circuit below contains a metal oxide rod, represented by a dashed line. The potential difference (in volts) across the rod is given by $V = 0.200I^2$ where I is the current (in amps) through the rod. This relationship is only valid for $I > 0$.

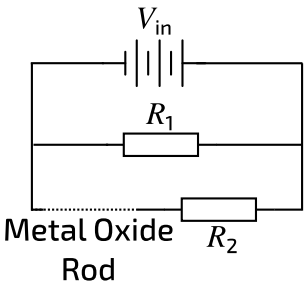


Figure 1: Circuit diagram showing how the rod, resistors and cell are connected to each other.

Given that $R_1 = 3.00\ \Omega$, $R_2 = 2.00\ \Omega$ and $V_{\text{in}} = 6.00\ \text{V}$ what is the total current drawn from the cell?

Adapted with permission from UCLES, A Level Physics, June 1961, Paper 3, Question 8

Gameboard:

STEM SMART Physics 30 - Complicated circuits

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.



Physics. *You work it out.*

[Home](#) [Gameboard](#) [Physics](#) [Electricity](#) [Resistors](#) [Transforming Resistors](#)

Transforming Resistors

A Level



The two resistor networks below can be called equivalent if they have the same electrical properties when viewed between any two of the terminals A , B or C . R_a , R_b and R_c can be given values based on the values of R_x , R_y and R_z in order to make the two networks equivalent.

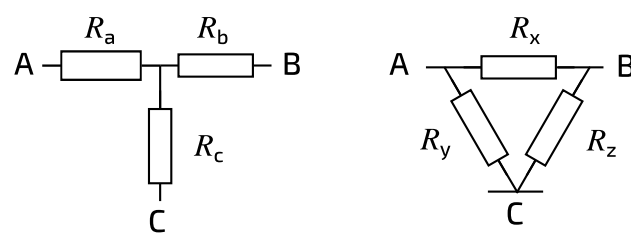


Figure 1: Two resistor networks.

Part A Expression for R_a

If the two resistor networks of **Figure 1** are equivalent, find an expression for R_a in terms of R_x , R_y and R_z .

The following symbols may be useful: R_a , R_x , R_y , R_z

Part B A circuit

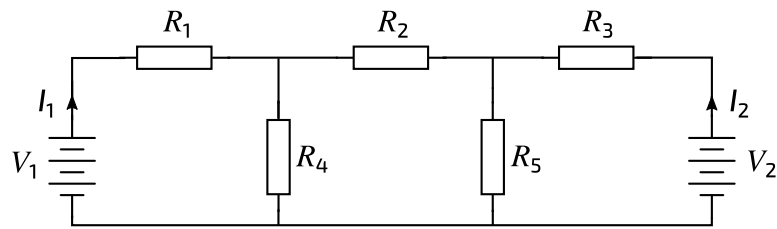


Figure 2: A circuit with two cells and five resistors.

Using the transformation and your result from Part A, or otherwise, work out the value of the current I_1 in the circuit of **Figure 2**. You are given that $R_1 = 1.0\ \Omega$, $R_2 = R_4 = R_5 = 3.0\ \Omega$, $R_3 = 2.0\ \Omega$, $V_1 = 22\ \text{V}$ and $V_2 = 11\ \text{V}$.

Created for isaacphysics.org by Dominic Lyons

Gameboard:

STEM SMART Physics 30 - Complicated circuits

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.



Physics. *You work it out.*

[Home](#) [Gameboard](#) [Physics](#) [Electricity](#) [Resistors](#) [Cube of Resistors](#)

Cube of Resistors

A Level



Imagine a cube of resistors, where each edge of the cube is a resistor of resistance $1\ \Omega$. In this question we will find the equivalent resistance between different vertices.

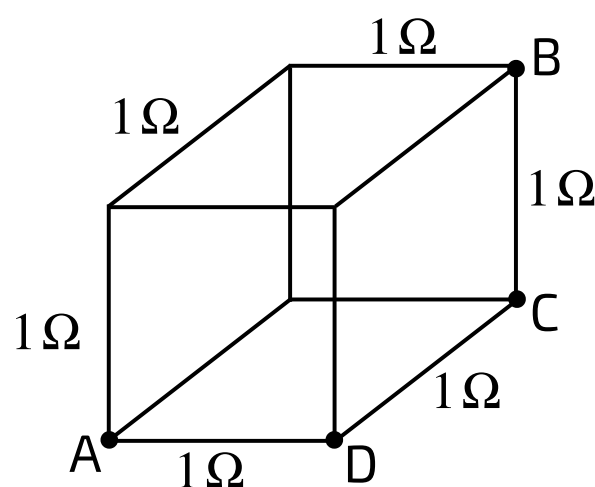


Figure 1: A cube of $1\ \Omega$ resistors. Six of the twelve edges are labelled; all have the same resistance. Four of the vertices are labelled.

Part A Resistance across main diagonal

What is the equivalent resistance between two vertices on the main diagonal, e.g. between points A and B in **Figure 1**? Give your answer to 3 s.f.

Part B Resistance across diagonal of a face

What is the equivalent resistance between two vertices on the diagonal of a face, e.g. between points A and C in **Figure 1**? Give your answer to 3 s.f.

Part C Resistance between adjacent vertices


What is the equivalent resistance between two adjacent vertices, e.g. between points A and D in **Figure 1**? Give your answer to 3 s.f.

Created for isaacphysics.org by Ben Blayney

Gameboard:

STEM SMART Physics 30 - Complicated circuits

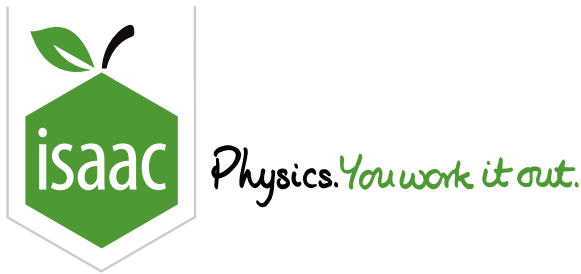All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.



Rambunctious Resistors

A Level
C C C

The circuit diagram below shows a combination of resistors with equivalent resistance $R_{eq} = 37.0\ \Omega$.

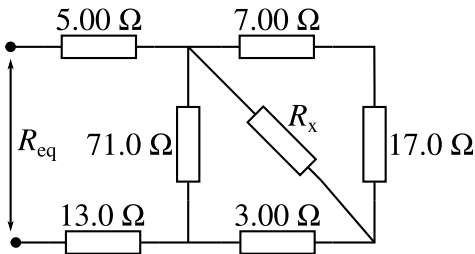


Figure 1: Circuit diagram showing how the resistors are arranged and the values of the resistances. The unknown resistor has resistance R_x .

What value of resistance R_x for the unknown resistor satisfies this value for the equivalent resistance?

Created for isaacphysics.org by Ben Blayney

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.