

## Current and Circuits

**Electric charges** travel round a circuit to create a \_\_\_\_\_.

Current is measured in \_\_\_\_\_ (A).

The charges can be \_\_\_\_\_ or \_\_\_\_\_. Electric charges are the \_\_\_\_\_ "material" in a circuit.

For \_\_\_\_\_ to flow around a circuit, the circuit must form a \_\_\_\_\_. We say it is \_\_\_\_\_.

If the circuit has a gap, it is **open**, and the current is \_\_\_\_\_.


1 Which of these four situations are open open circuits and which are closed circuits?

(a) The bedside lamp is off.




(c) The toaster is toasting bread.

(b) The phone is charging.



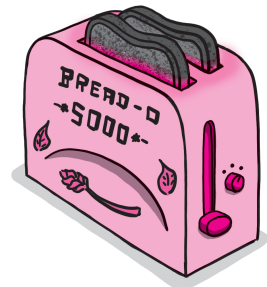
(d) A remote control has a missing battery.



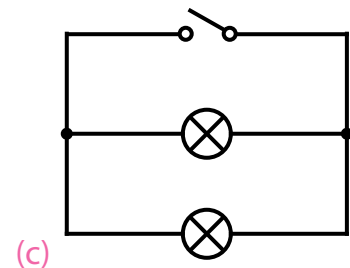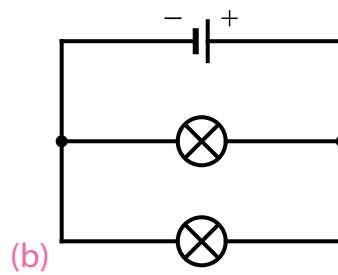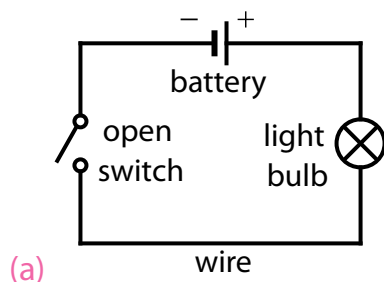2 Which of these circuits are open and which are closed?




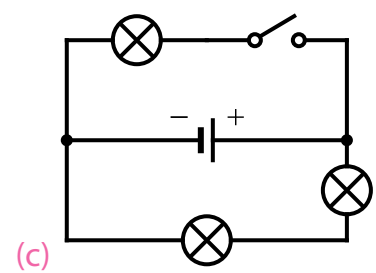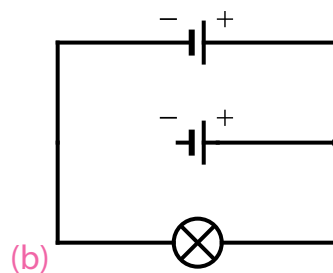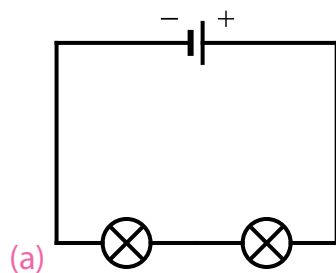3 Draw around the closed loop in these circuits.






The direction of the \_\_\_\_\_ in circuits is the same as the \_\_\_\_\_ in which \_\_\_\_\_ charges would move.



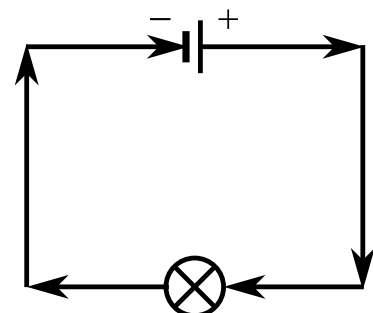
\_\_\_\_\_ charges will be \_\_\_\_\_ (pushed away) from the \_\_\_\_\_ (+) terminal of the battery. They are \_\_\_\_\_ to (pulled towards) the \_\_\_\_\_ (-) terminal of the battery.



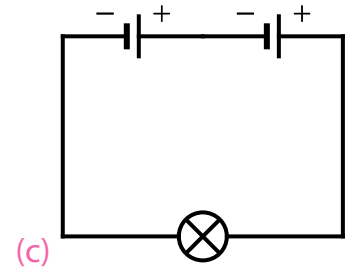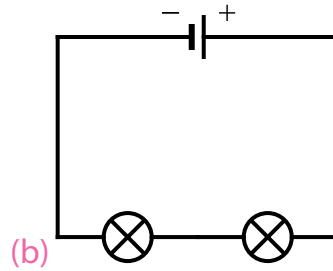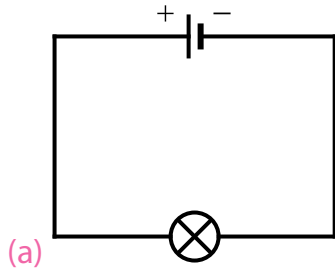
4 Draw arrows on the circuits in the direction of the current.




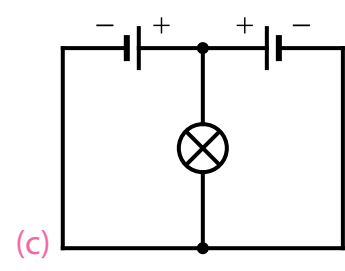
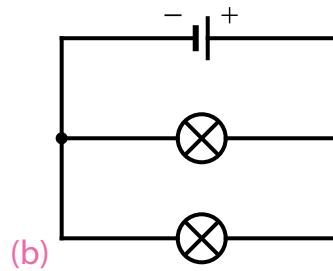
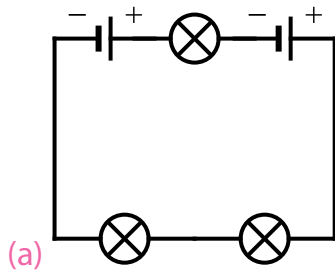
5 Draw arrows on the circuits in the direction of the current. Each line needs an arrow.



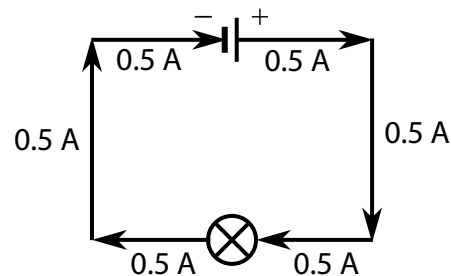
Charges in a \_\_\_\_\_ cannot be \_\_\_\_\_. The **total** amount of \_\_\_\_\_ in a \_\_\_\_\_ circuit is the \_\_\_\_\_ at all points. This is an important rule of charge and current.



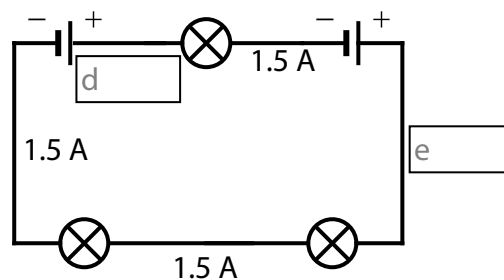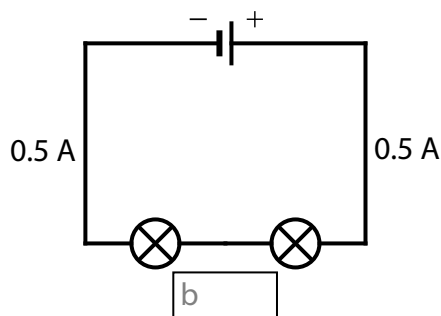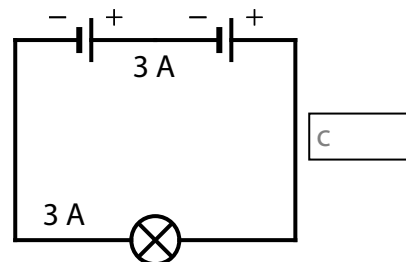
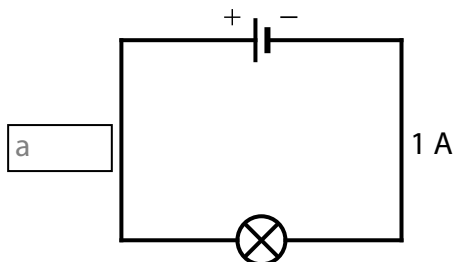
6 Write down the current in each of the boxes.



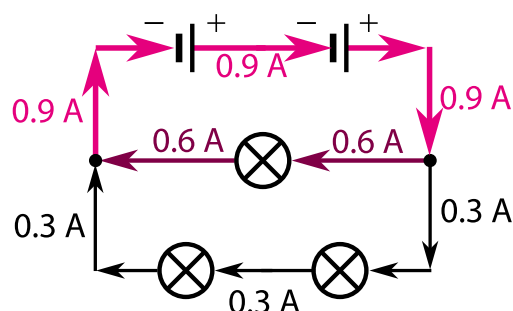
\_\_\_\_\_ circuits have \_\_\_\_\_. The \_\_\_\_\_ current \_\_\_\_\_ a junction must be the \_\_\_\_\_ as the \_\_\_\_\_ current \_\_\_\_\_ of the junction.



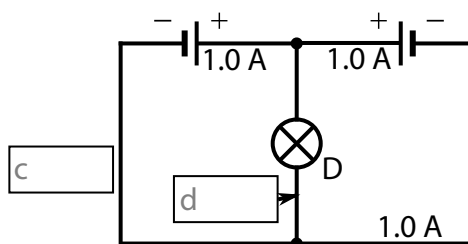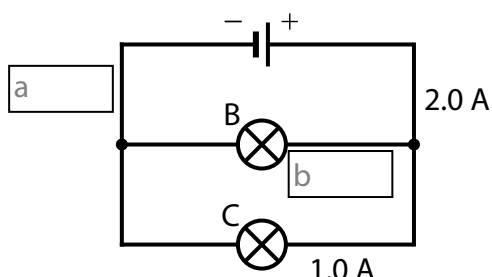7 Write down the current in each of the boxes on these circuits from question 5.



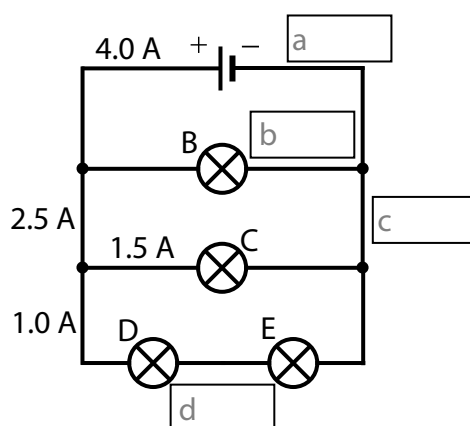8 Write down the current in each of the boxes.



If two light bulbs are on the \_\_\_\_\_ of the circuit, we say they are in \_\_\_\_\_. The \_\_\_\_\_ is the \_\_\_\_\_ through each bulb.

If two light bulbs are on \_\_\_\_\_ of the circuit, we say the bulbs are in \_\_\_\_\_. The \_\_\_\_\_ is \_\_\_\_\_ between the two \_\_\_\_\_ of the circuit.

When \_\_\_\_\_ passes through a \_\_\_\_\_, the bulb \_\_\_\_\_. For a circuit with identical light bulbs, the \_\_\_\_\_ one is carrying the most \_\_\_\_\_.

9 Fill in the sentences with the words **same**, **shared**, **most**, **brightness**.

(a) The current through two identical light bulbs in **series** will be the \_\_\_\_\_. They will have the same \_\_\_\_\_.

(b) The current through light bulbs in **parallel** will be \_\_\_\_\_. The branch with the \_\_\_\_\_ current passing through it will have the **brightest** light bulbs.

10 Go back to the circuits in questions 7 and 8. The light bulbs are identical in those circuits. Label which light bulbs will have the **same brightness**, which will be **brightest** and which will be **dimpest**.