



Physics. *You work it out.*

# Further Electricity

A-level overview

[isaacphysics.org](https://isaacphysics.org)

[https://isaacphysics.org/pages/remote\\_learning](https://isaacphysics.org/pages/remote_learning)



# Alternating Current





# Direct and alternating current

Batteries and cells give direct current


The voltage is constant

The mains (made by coils of wire rotating in magnetic fields) is alternating current.

The voltage varies in time like the position of an oscillator

$$V = V_{pk} \cos(\omega t)$$

The mean voltage is zero

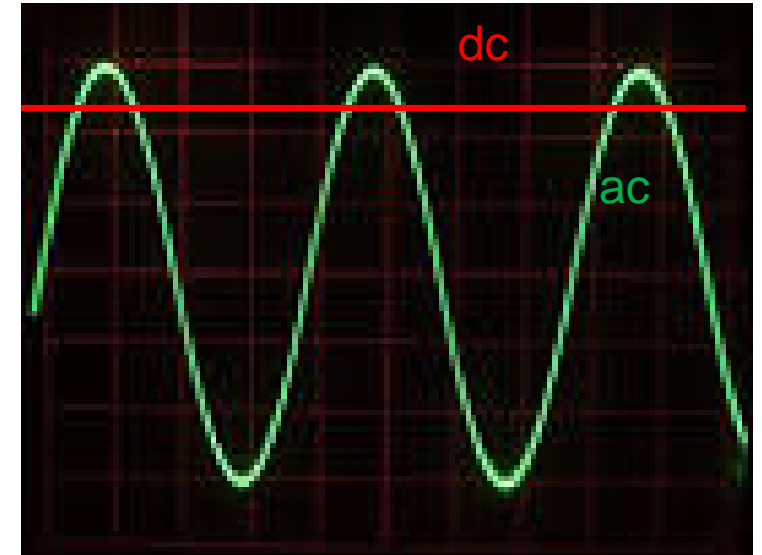



# Power in a.c.

If

$$V = V_{pk} \cos(\omega t)$$

then the current


$$I = \frac{V}{R} = \frac{V_{pk}}{R} \cos(\omega t)$$

and the power

$$P = VI = \frac{V_{pk}^2}{R} \cos^2(\omega t)$$

so average power
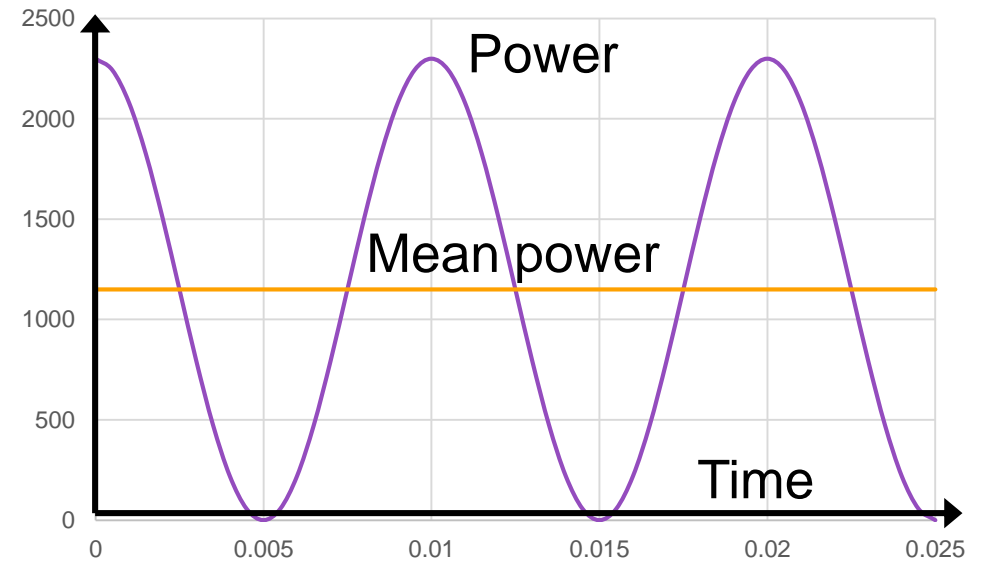
$$P_{av} = \frac{V_{pk}^2}{2R} = \frac{1}{R} \left( \frac{V_{pk}}{\sqrt{2}} \right)^2$$



which is the same as the power delivered by a d.c. voltage  $V_{rms} = \frac{V_{pk}}{\sqrt{2}}$




# RMS

For UK mains,

$$V_{\text{rms}} = 230\text{V so } V_{\text{pk}} = 325\text{V}$$

$$f = 50\text{Hz}$$

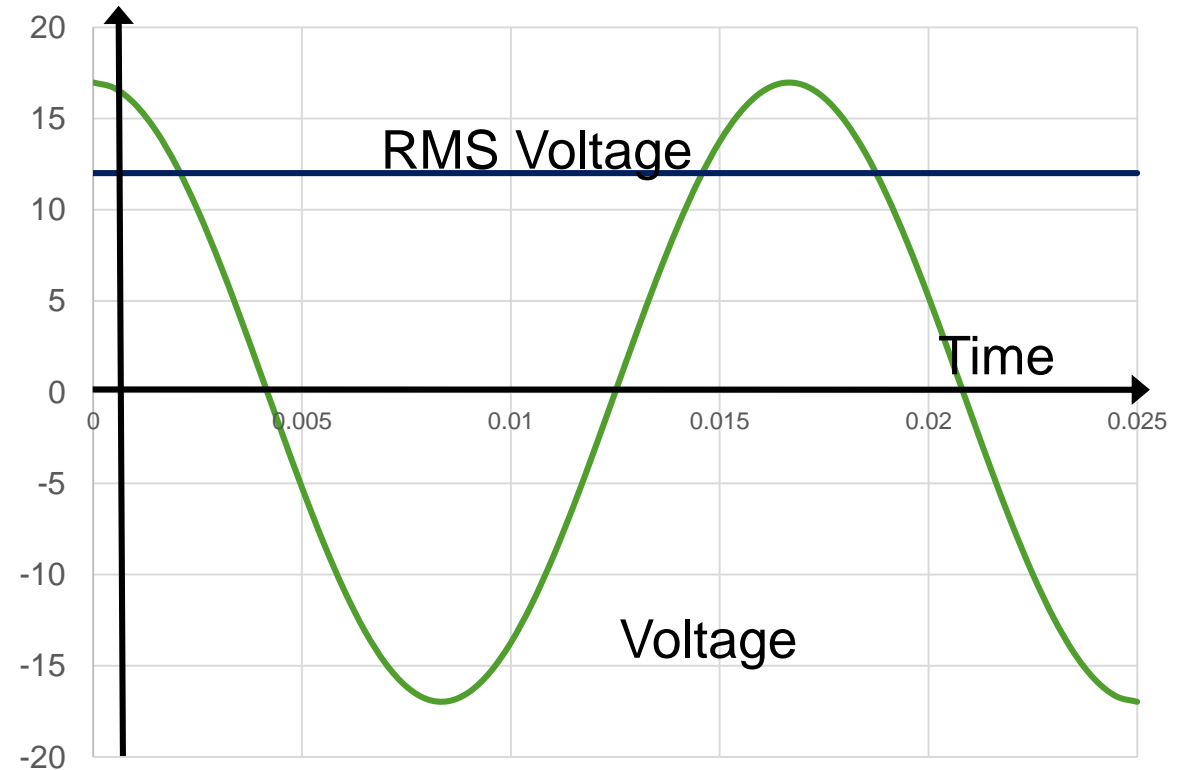
If you use RMS values for current and voltage and mean value for power, d.c. equations  $P=IV$ ,  $P=I^2R$  etc still work.



RMS means 'root mean square'

$$V_{\text{rms}} = \text{square root of the average of } V^2$$

# Oscilloscopes

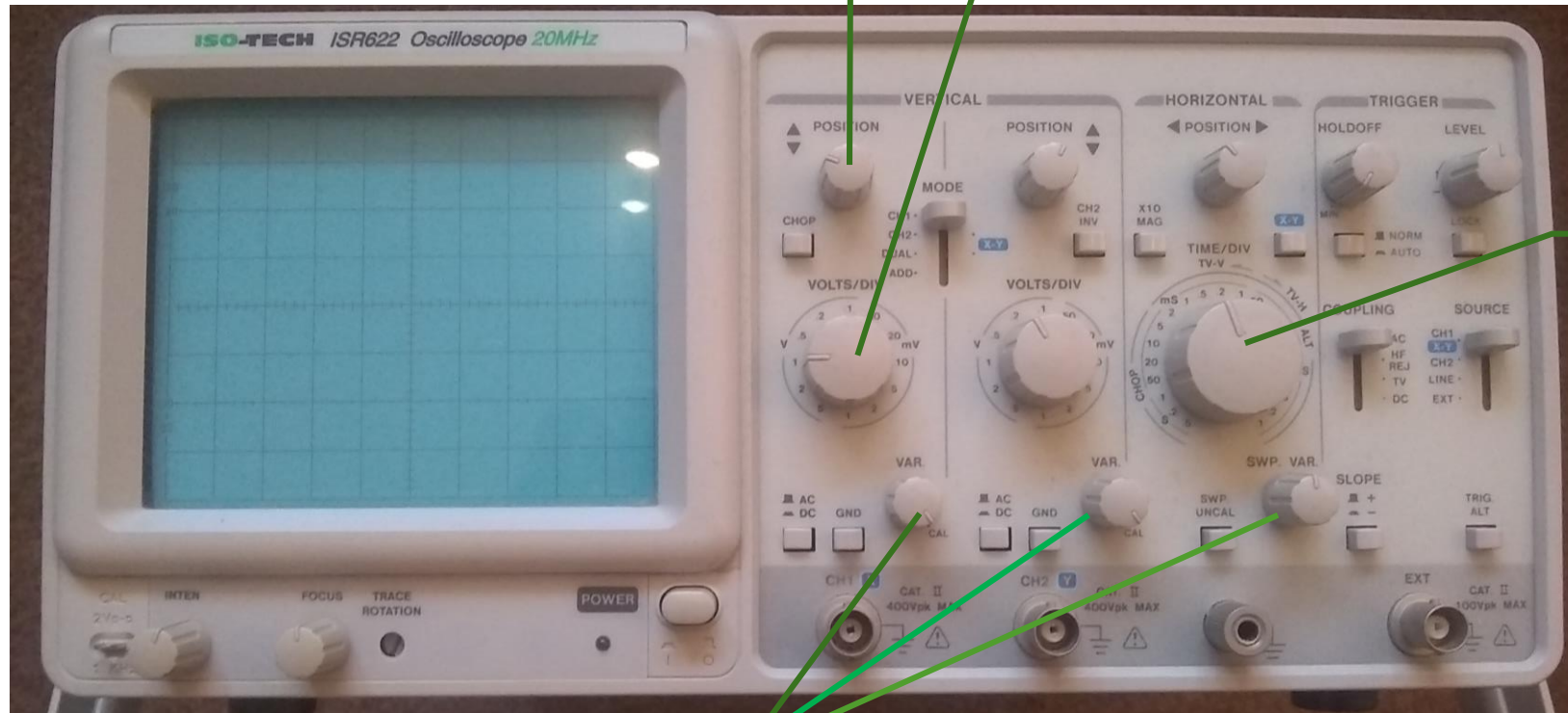


y-pos  
Moves trace up and down

Sensitivity  
V/div on vertical

Time base  
s/div on horizontal

Variable sensitivity  
set to CAL

# Alternating current practice

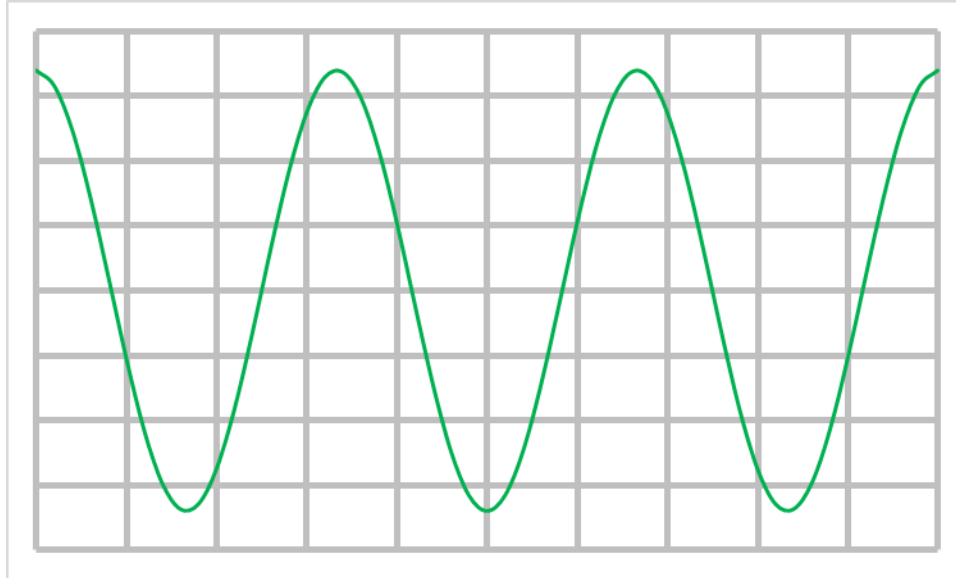

An oscilloscope is set to a y-gain of 2V/div and a time base of 20ms/div

From this trace, work out the frequency, the RMS voltage and the power if this were connected to a  $12\Omega$  resistor.


# Capacitors







# Introducing capacitors

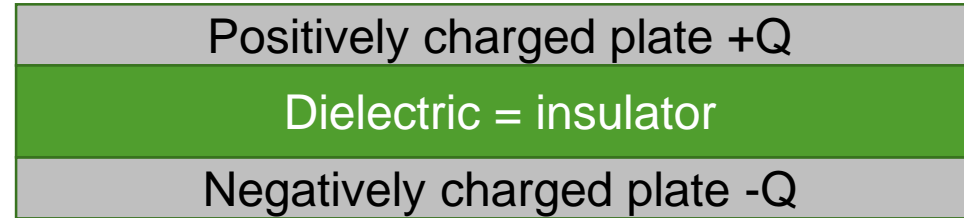

In a capacitor charge is separated

Charge 'stored' is proportional to voltage

$$Q = CV$$


$C$  is capacitance, measured in farads F.  $1F = 1C/V$

Often, capacitors are measured in  
 $\mu F = 10^{-6}F$ ,  $nF = 10^{-9}F$ , or  $pF = 10^{-12}F$

Energy stored = area under  $V$  vs  $q$  graph


$$U = \frac{1}{2}QV = \frac{1}{2}CV^2$$

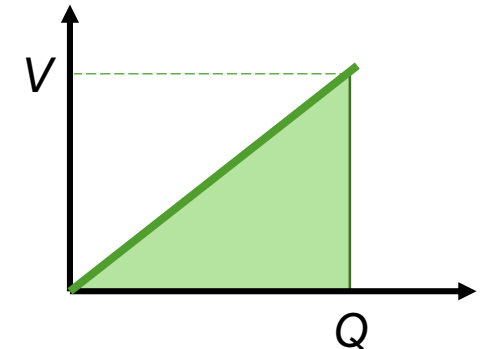**Always connect  
capacitor with correct  
polarity**





# Capacitance and field

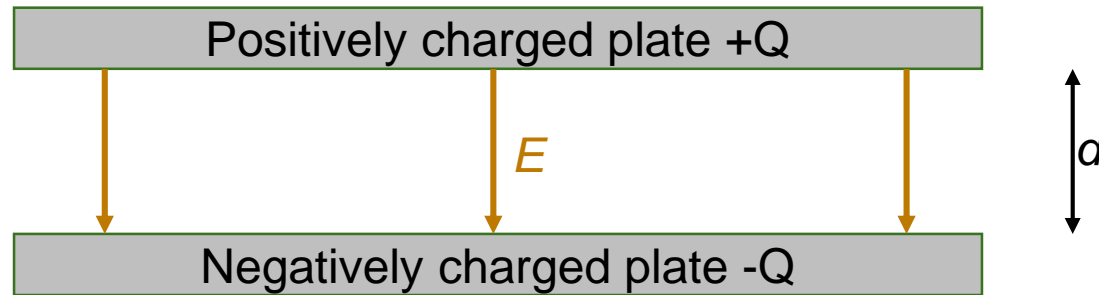

Field proportional to charge  $\epsilon EA = Q$

Electric field related to voltage  $E = \frac{V}{d}$

$$Q = \epsilon EA = \epsilon \frac{VA}{d} \quad C = \frac{Q}{V} = \frac{\epsilon A}{d}$$



## Capacitor practice

1. Calculate the charge stored on a  $20\text{nC}$  capacitor connected to a  $6.5\text{V}$  battery.
2. Calculate the energy stored in the capacitor in q1.
3. Calculate the capacitance needed to store  $2.5\text{J}$  at  $12\text{V}$ .





# Capacitor networks

- › Capacitors in parallel: like resistors in series

$$C_{TOT} = C_1 + C_2$$

- › Capacitors in series: like resistors in parallel

$$C_{TOT} = (C_1^{-1} + C_2^{-1})^{-1}$$

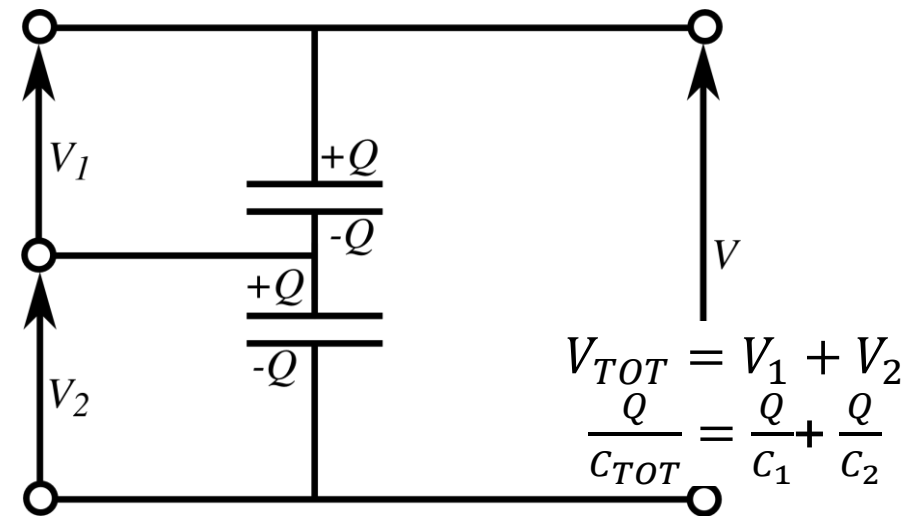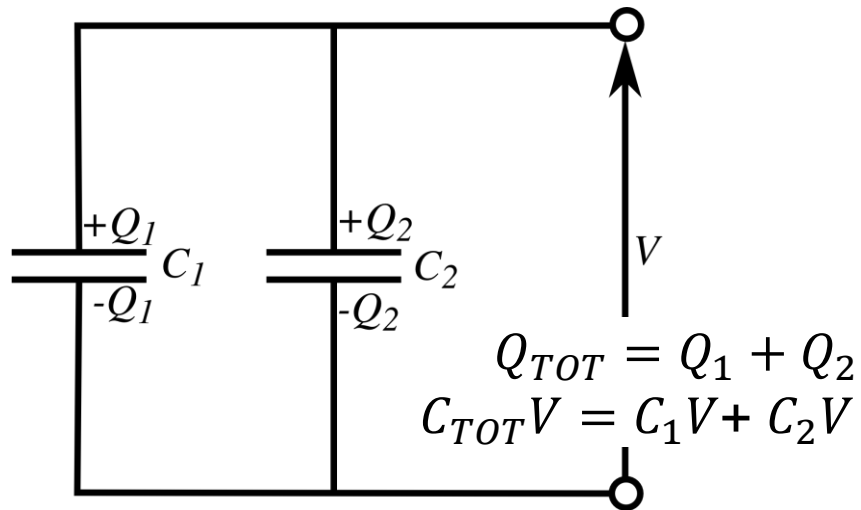



## Example

- › A  $1000\mu\text{F}$  capacitor is charged using a 10V battery.
- › It is then connected to an uncharged  $500\mu\text{F}$  capacitor.
- › What is the new voltage?




## Capacitor network practice

1. Calculate the capacitance of 4nF, 10nF and 15nF capacitors connected in parallel.
2. Calculate the capacitance of a 24 $\mu$ F capacitor connected in series with a 16 $\mu$ F capacitor.
3. A 220 $\mu$ F capacitor is connected to a 12V battery, it is then connected in parallel with an uncharged 630 $\mu$ F capacitor. What is the voltage now?



# Time constant

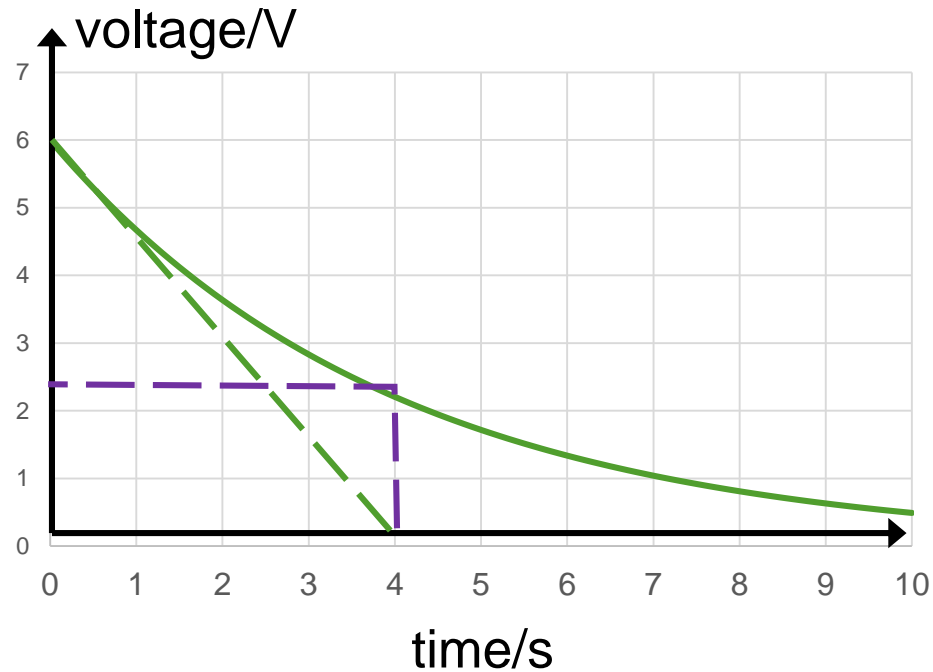

After one time constant,  
voltage has fallen to  $\frac{V_0}{e} \approx$   
 $0.37V_0$

- › Initial discharge current

$$I_0 = \frac{V_0}{R} = \frac{Q_0}{RC}$$


- › If this current were constant, the capacitor would discharge in time constant

$$t = \frac{Q_0}{I_0} = RC$$

- › During discharge,  $Q$  drops so  $V = \frac{Q}{C}$  drops, so  $I = \frac{V}{R} = \frac{Q}{RC}$  drops and rate of discharge falls

# Capacitor discharge

$$I = \frac{V}{R} = \frac{Q}{RC}$$

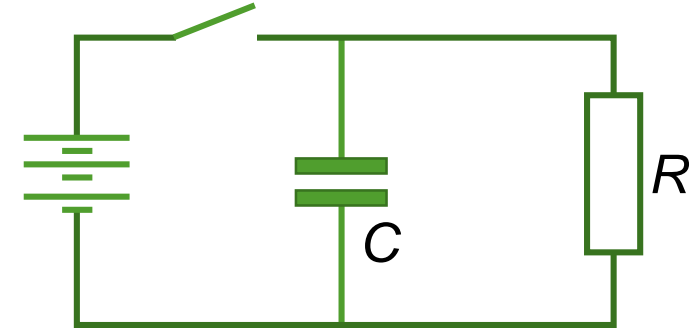

If  $I=0.05\text{A}$ , then  $Q$  gets smaller by  $0.05C$  each second,  
thus

$$I = -\frac{dQ}{dt} = \frac{Q}{RC}$$

**Solution**

$$I = I_0 e^{-\frac{t}{RC}}, \quad V = V_0 e^{-\frac{t}{RC}}, \quad Q = Q_0 e^{-\frac{t}{RC}}$$





## Solving for time

$$V = V_0 e^{-\frac{t}{RC}}, \quad \frac{V}{V_0} = e^{-\frac{t}{RC}}$$

taking natural logarithms ( $\ln 1 = 0$ ,  $\ln e = 1$ ,  $\ln e^2 = 2$ ,  $\ln e^3 = 3$ )

$$\ln \frac{V}{V_0} = -\frac{t}{RC}$$

If voltage has halved,  $V_0 = 2V$ , and

$$\ln \frac{1}{2} = -\frac{t}{RC} \quad -0.693 = -\frac{t}{RC} \quad t = 0.693 RC$$



## Capacitor discharge practice

1. Calculate the time constant of a circuit containing a  $2200\mu\text{F}$  capacitor and a  $200\text{k}\Omega$  resistor.
2. What is the initial discharge current if the capacitor in q1 starts with a voltage of 12V?
3. What will the discharge current be 880s after the start?
4. When will the voltage have dropped to 10V?



# Links

## A Level Topic Revision



[https://isaacphysics.org/pages/  
a\\_level\\_topic\\_index#a\\_level\\_revision](https://isaacphysics.org/pages/a_level_topic_index#a_level_revision)

## Consolidation Programme



[https://isaacphysics.org/pages/  
summer\\_programmes\\_2021](https://isaacphysics.org/pages/summer_programmes_2021)