



Truth table for logic gate 1

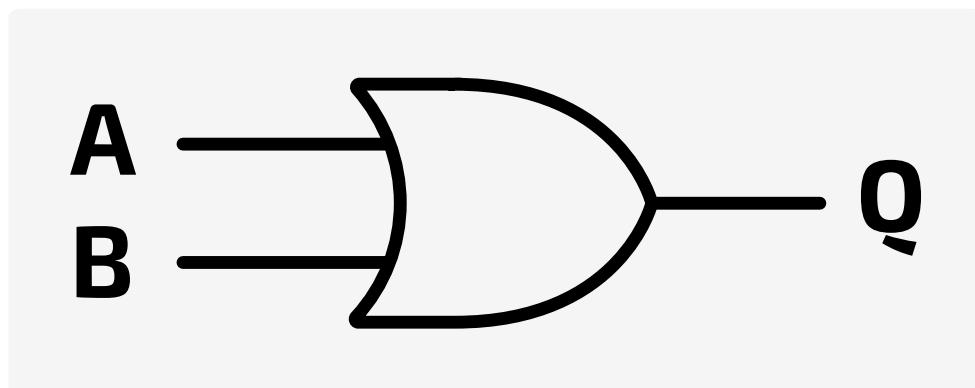


Figure 1: A logic gate

Select the correct truth table for the logic gate represented by the symbol in Figure 1.

☐

A	Q
0	1
1	0

☒

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

☐

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

☐

A	B	Q
0	0	0
0	1	0

1	0	0
1	1	1

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.



Select logic gate from truth table 3

Practice 1

Which logic gate does the truth table below represent?

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

- ☐ NAND
- ☒ XOR
- ☐ OR
- ☐ NOR

Quiz:
STEM SMART Computer Science Week 2

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.



Complete truth table for logic circuit 3



Study the logic circuit shown in **Figure 1** and the truth table below.

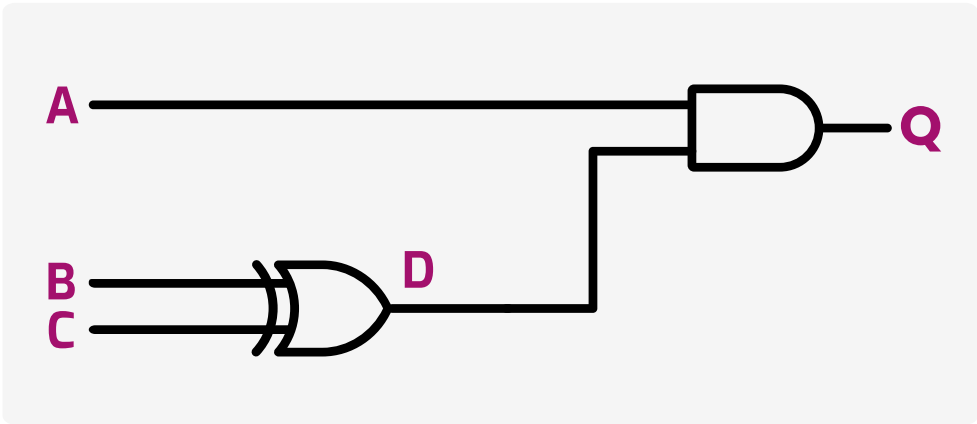


Figure 1: A circuit diagram

Complete the truth table for the logic circuit diagram in **Figure 1**. The column **D** represents the output of the logic gate with inputs B and C. The final output is in column **Q**.

A	B	C	D	Q
0	0	0	<input type="text"/>	<input type="text"/>
0	0	1	<input type="text"/>	<input type="text"/>
0	1	0	<input type="text"/>	<input type="text"/>
0	1	1	<input type="text"/>	<input type="text"/>
1	0	0	<input type="text"/>	<input type="text"/>
1	0	1	<input type="text"/>	<input type="text"/>
1	1	0	<input type="text"/>	<input type="text"/>
1	1	1	<input type="text"/>	<input type="text"/>



Boolean operator precedence 2

Boolean operators have an order of precedence which is taken into account when an expression is evaluated. Some operators have equal precedence.

The groups below contain **sets of operators with equal precedence**. Drag the groups into order so that the group with the highest precedence is at the top, and the group with the lowest precedence is at the bottom.

Available items

Your answer

BRACKETS

NOT

AND, NAND

OR, NOR, XOR

Quiz:

STEM SMART Computer Science Week 2

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.






Logic circuit for a problem


A water sprinkler (W) is on when the timer (T) is set, the temperature (C) exceeds 26° Celsius, and the rain sensor (R) does not detect rainfall.

- The timer (T) is 1 when it has been set
- The temperature sensor (C) is 1 when the temperature is over 26° Celsius
- The rain sensor (R) is 1 when rainfall is detected

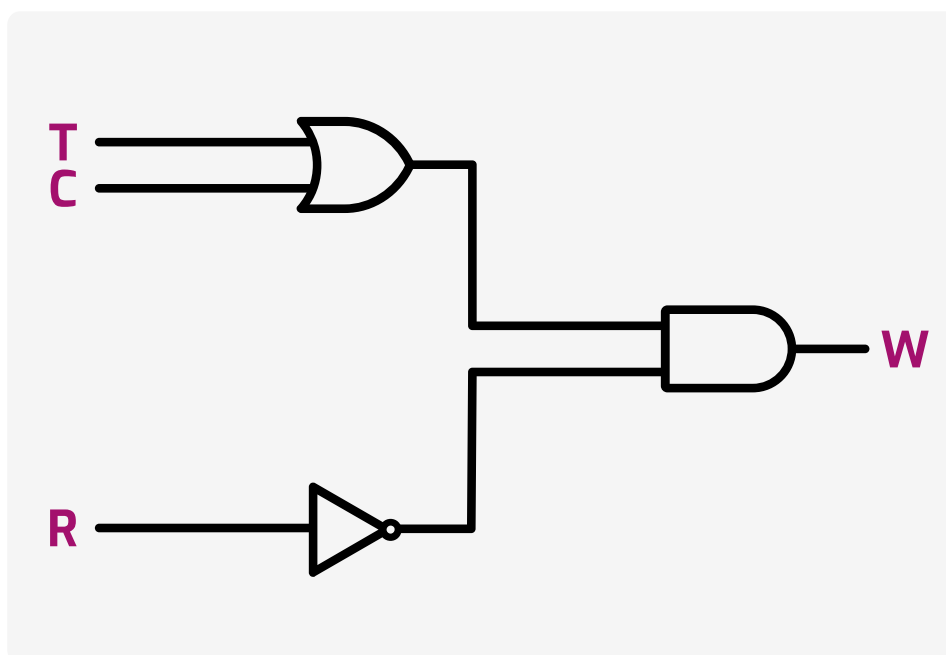
Select the logic circuit diagram that corresponds to the circuit for the sprinkler.




Option A circuit diagram

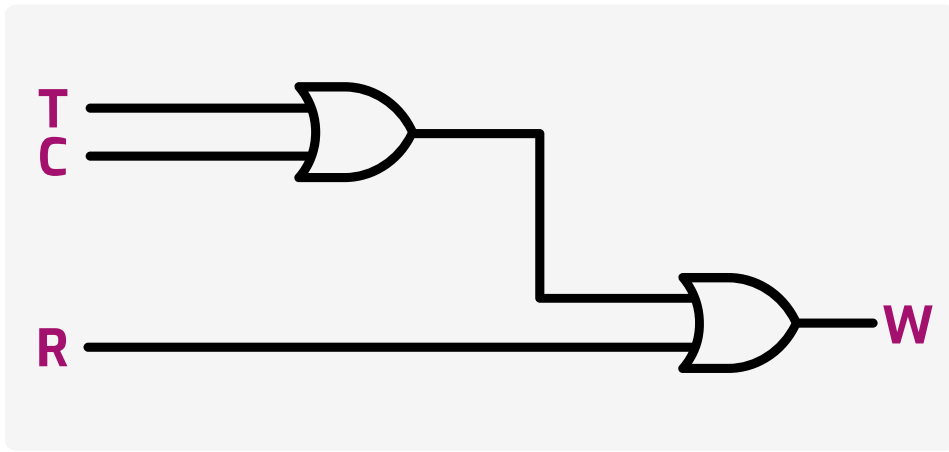

Option B circuit diagram

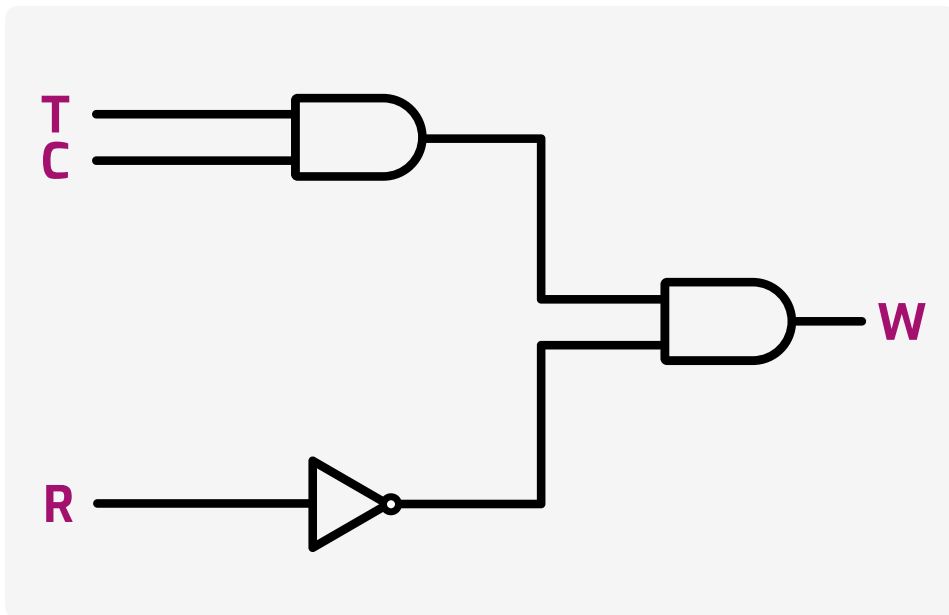

Option C circuit diagram

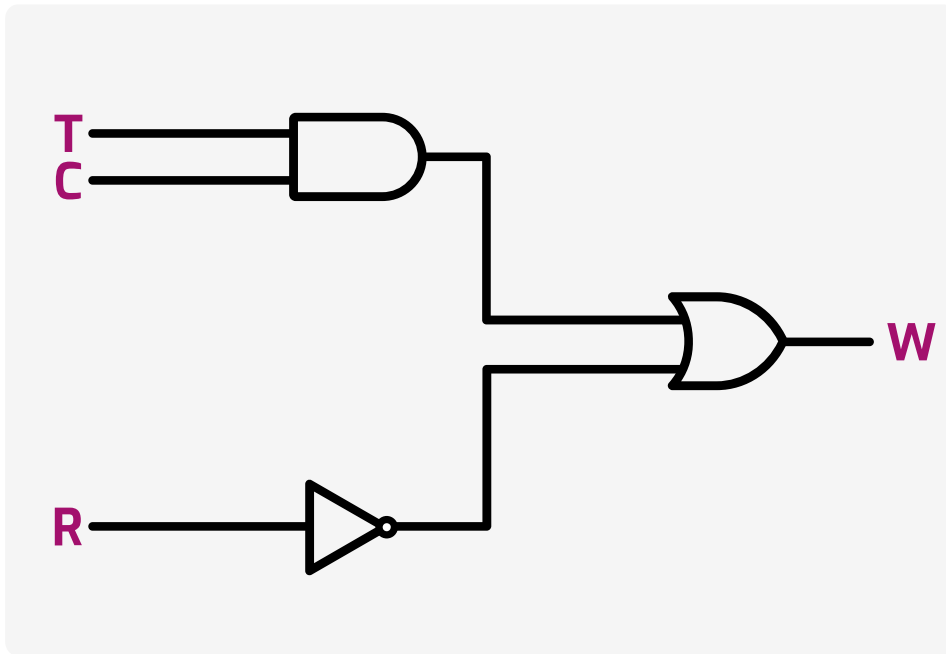

Option D circuit diagram

Select the correct logic diagram for the sprinkler.

- ☐ Option A
- ☐ Option B
- ☒ Option C
- ☐ Option D

Quiz:

STEM SMART Computer Science Week 2

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.







Logic circuit for expression

Which of the circuits below represents the following Boolean expression?

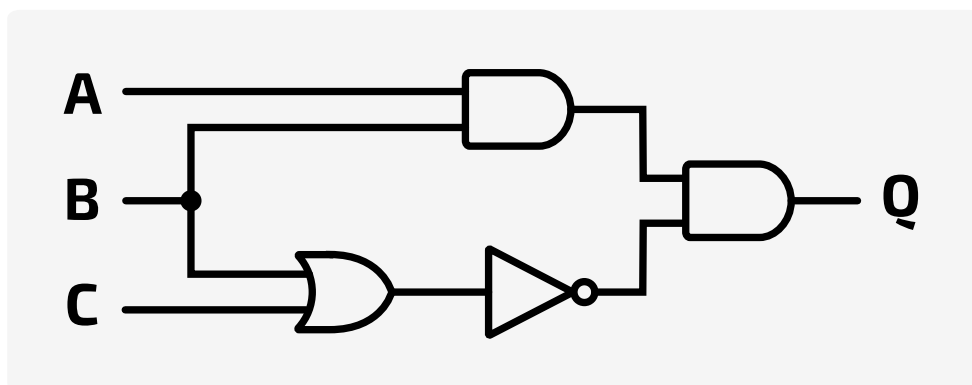
$$Q = (A \cdot B) \cdot (\overline{C} + B)$$




Option A

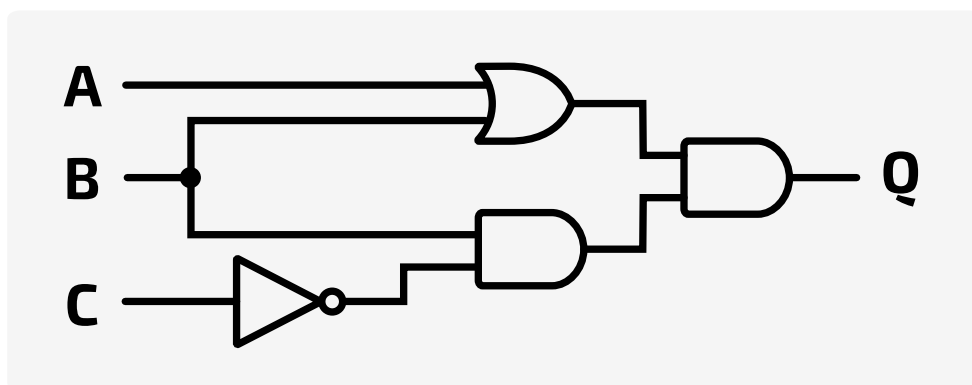

Option B

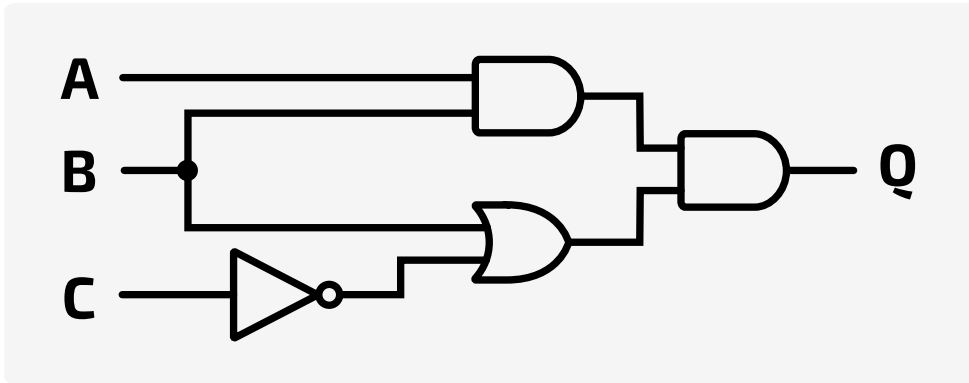

Option C

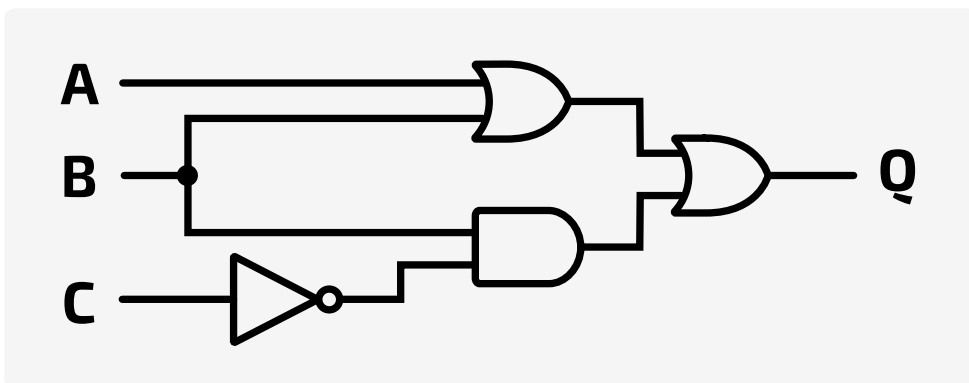

Option D

- ☐ Option A
- ☐ Option B
- ☒ Option C
- ☐ Option D

Quiz:

STEM SMART Computer Science Week 2

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.





Expression for truth table 3

Select the Boolean expression that corresponds to this truth table:

INPUTS		OUTPUT
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Select the correct Boolean expression for the given truth table.

- ☐ $Q = A \text{ AND } (\text{NOT } B)$
- ☐ $Q = (\text{NOT } A) \text{ OR } B$
- ☒ $Q = \text{NOT}(A \text{ AND } B)$
- ☐ $Q = \text{NOT } (A \text{ OR } B)$

Quiz:

STEM SMART Computer Science Week 2

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.



Expression for problem 1

Challenge 2



The offices at the Raspberry Pi Foundation have a security alarm that is set automatically each evening at 6.00pm. If the alarm is armed and a person is detected in the building, the alarm sounds (really loudly!).

Sensing that there could be a problem with the automatic alarm, the clever technicians at Raspberry Pi made it so that the alarm will not be armed at 6.00pm if someone is still in the building. Instead, there is a manual switch that can be used to set the alarm once the last person leaves.

- The evening time (E) is set to True when it is 6.00pm.
- The person detector (P) is set to True when someone is in the building.
- The manual switch (M) is set to True when the alarm is turned on manually.

Complete the Boolean expression for the alarm (A) to be set to True (and armed) when it is manually switched on, or if everyone has left the building at 6.00pm.

The following symbols may be useful: A , E , M , P

Quiz:

[STEM SMART Computer Science Week 2](#)

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.





Truth table to match problem 1

Lucia has made a circuit to control her garden lights. The circuit will have a switch, a light sensor, and a rain sensor. The lights will come on when the lights are switched on or the light sensor detects that it is sufficiently dark. They will not come on at all if it is raining.

- The switch (S) returns 1 when the switch is set on
- The light sensor (L) returns 1 when it is light outside
- The rain sensor (R) returns 1 when it is raining

When the input to the garden lights (G) is 1, the lights will turn on.

Which of the following options shows the truth table for the circuit?

☐

S	L	R	G
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

☐

S	L	R	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

○

S	L	R	G
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

○

S	L	R	G
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 Quiz:

STEM SMART Computer Science Week 2

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.





Truth table for expression

A truth table can be used to check the logic of a Boolean expression. Consider the following expression:

$$Q = R + (S \cdot \overline{T})$$

Create a truth table for the expression. There are three rows in the truth table which produce an output (Q) of 0. What are the values of R , S , and T for these three rows?

☒ $R = 0; S = 0; T = 0$

$R = 0; S = 0; T = 1$

$R = 0; S = 1; T = 1$

☐ $R = 1; S = 0; T = 1$

$R = 1; S = 1; T = 0$

$R = 1; S = 1; T = 1$

☐ $R = 1; S = 0; T = 1$

$R = 1; S = 0; T = 1$

$R = 1; S = 1; T = 0$

☐ $R = 0; S = 0; T = 0$

$R = 0; S = 0; T = 1$

$R = 0; S = 1; T = 0$

All teaching materials on this site are available under a CC BY-NC-SA 4.0 license, except where otherwise stated.

