

Current and Circuits

Electric charges travel round a circuit to create a **current**. Current is measured in **Amps** (A). The charges can be **positive** or **negative**.

Electric charges are the **electrical** "material" in a circuit.

For a **current** to flow in a circuit, the circuit must form a **loop**. We say it is **closed**.

If the circuit is **open**, the current is **zero**.

1 Which of these four situations are closed circuits?




(a) The bedside lamp is off.

(c) The toaster is toasting bread.




(b) The phone is charging.

(d) A remote control has a missing battery.

2 Which of these circuits are closed?

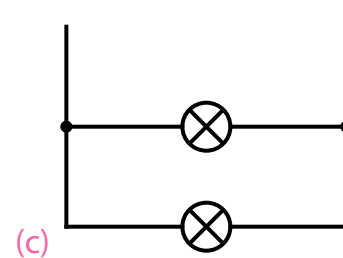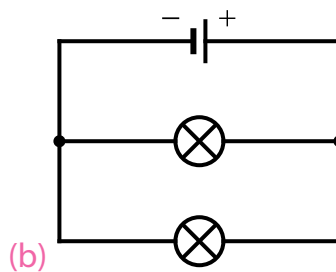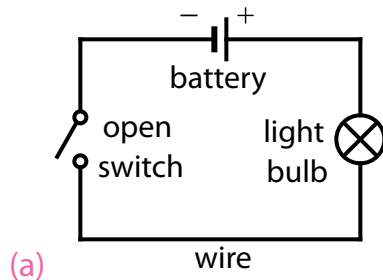


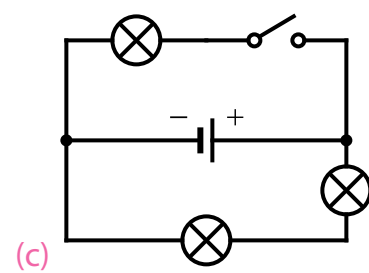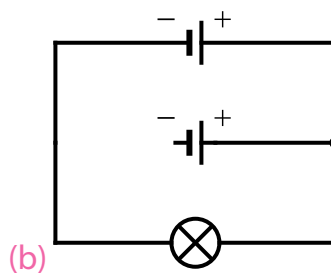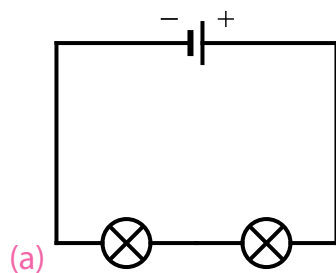3 Draw around the closed loop in these circuits.






The direction of the **current** in circuits is the same as the **direction** in which **positive** charges would move.



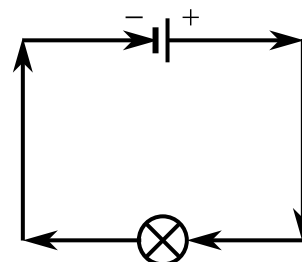
Positive charges will be **repelled** (pushed away) from the **positive** (+) terminal of the battery. They are **attracted** to (pulled towards) the **negative** (−) terminal of the battery.



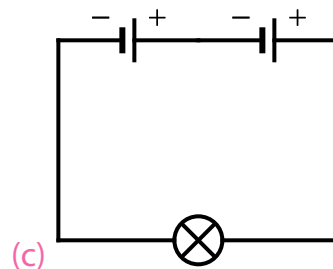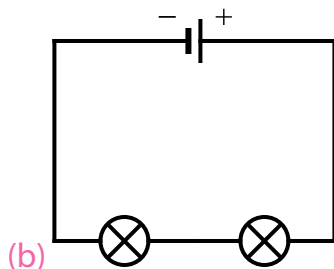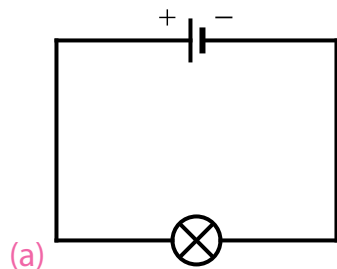
4 Draw arrows on the circuits in the direction of the current.




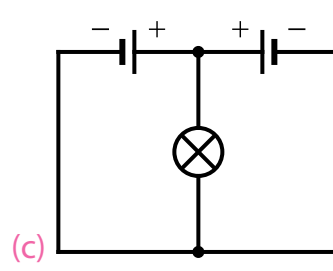
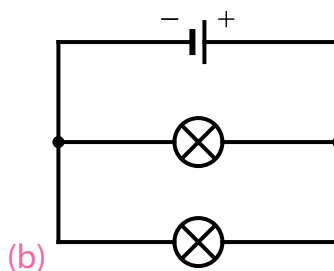
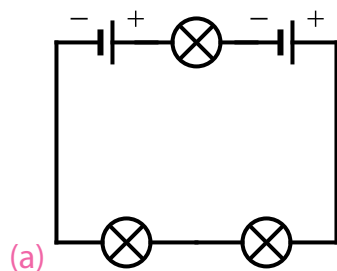
5 Draw arrows on the circuits in the direction of the current. Each line needs an arrow.



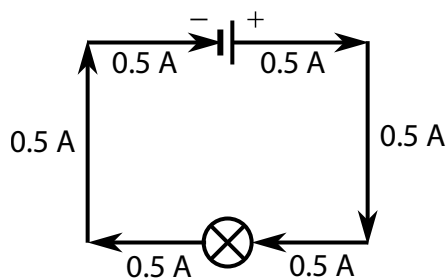Similar to energy, current is **never used up**. The total amount of **current** in a **closed** circuit stays the **same** in all parts of the circuit at one time. This is an important rule of charge and current.




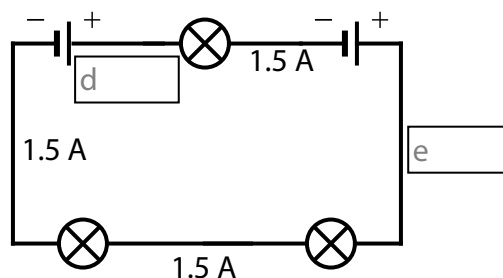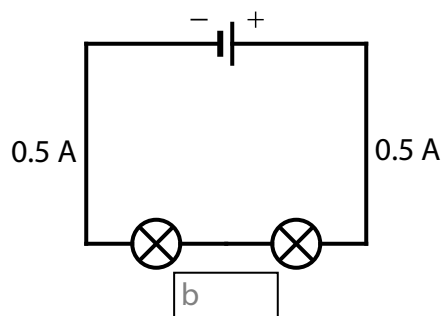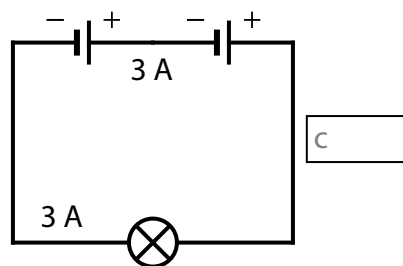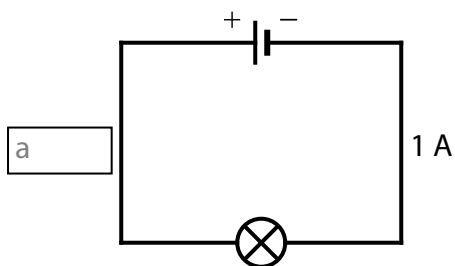6 Write down the current in each of the boxes.




(e)

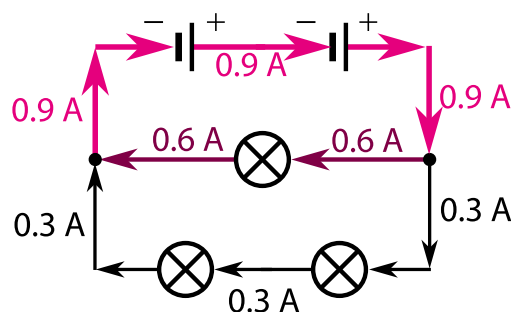
Parallel circuits have **junctions**. The **total** current **flowing into** a junction must be the **same** as the **total** current **flowing out** of the junction.



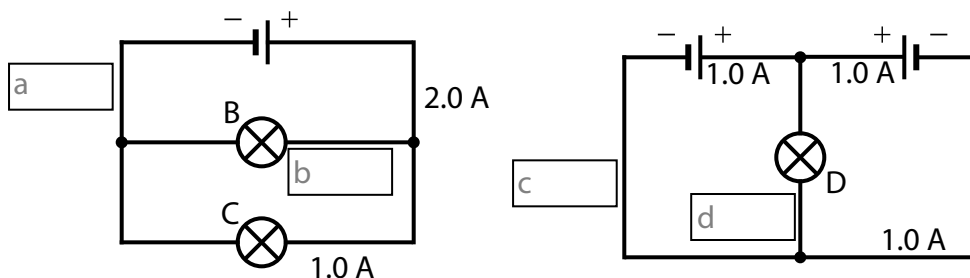7 Write down the current in each of the boxes on the circuits from question 5.



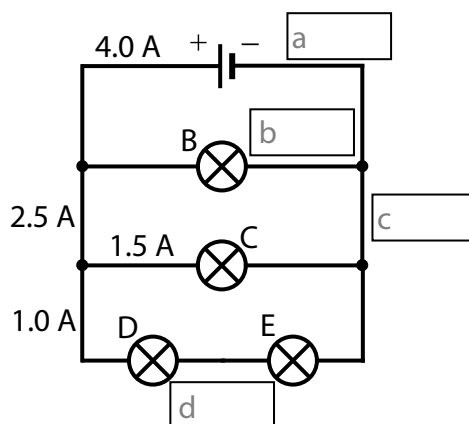8 Write down the current in each of the boxes.



If **two** light bulbs are **next** to each other on the **same branch** of the circuit, we say they are in **series**. The **current** is the **same** between the two.

If **two** light bulbs are on **different branches** of the circuit, we say the **bulbs** are in **parallel**. The **current** is **shared** through the two **branches** of the circuit.

When **current** moves through a **light bulb**, the bulb **lights up**. For identical light bulbs, the **more** current flowing through a bulb, the **brighter** it will be.

9 Fill in the sentences with the words **same**, **shared**, **most**, **brightness**.

(a) The current through two identical light bulbs in **series** will be the _____. They will have the same _____.

(b) The current through identical light bulbs in **parallel** will be _____. The bulb with the _____ current will be the brightest.

10 Go back to the circuits in questions 7 and 8. The light bulbs are identical in those circuits. Label which light bulbs will have the same brightness, which will be brightest and which will be dimmest.