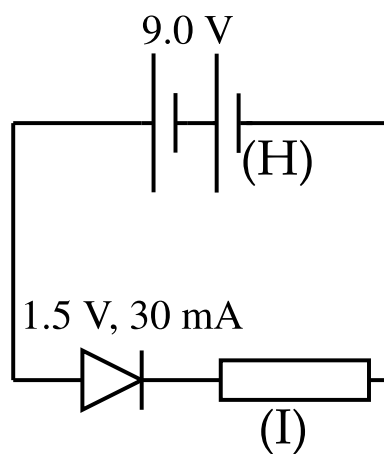


# Kirchhoff's Laws 4

Essential Pre-Uni Physics C4.4



**Figure 1:** Circuit diagram

## Part A Current in (H)

What is the current in (H)?

## Part B Current in (I)

What is the current in (I)?

---

## Part C Voltage across (I)

What is the voltage across (I)?

---


All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.

# Kirchhoff's Laws 3

Essential Pre-Uni Physics C4.3

**GCSE**  

**A Level**  

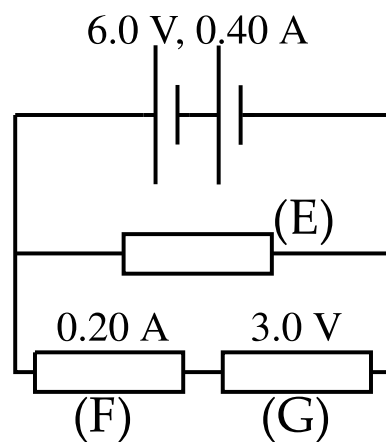**Figure 1:** Circuit diagram

## Part A Current in (E)

What is the current in (E)?

## Part B Voltage across (E)

What is the voltage across (E)?

## Part C Voltage across (F)

What is the voltage across (F)?

---

## Part D    Current in (G)

What is the current in (G)?

---

Gameboard:

**STEM SMART Physics Week 2 - Circuits**

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.

# Kirchhoff's Laws 5

Essential Pre-Uni Physics C4.5

GCSE

P

P

P

A Level

P

P

P

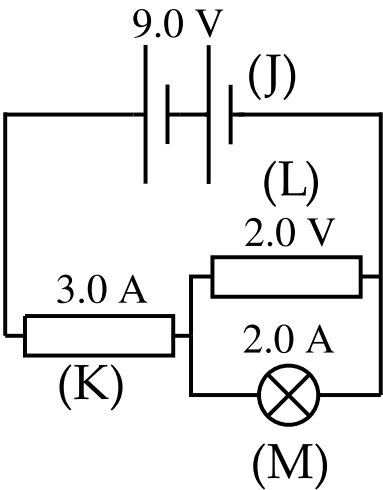


Figure 1: Circuit diagram

Part A    Current in (J)

What is the current in (J)?

Part B    Voltage across (K)

What is the voltage across (K)?

Part C    Current in (L)

What is the current in (L)?

---

## Part D Voltage across (M)

What is the voltage across (M)?

---

Gameboard:


**STEM SMART Physics Week 2 - Circuits**

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.

# Potential Dividers 1

Essential Pre-Uni Physics C5.1

---

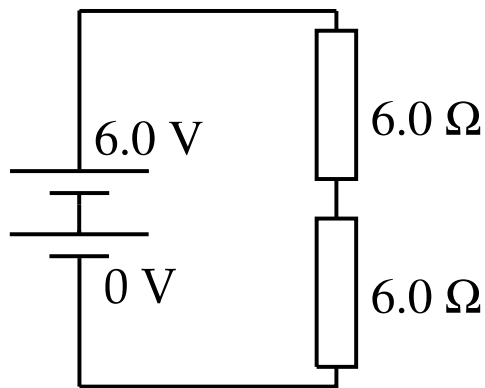

**Figure 1:** Circuit diagram

What is the voltage across the lower resistor in the circuit?

---

Gameboard:

**STEM SMART Physics Week 2 - Circuits**

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.




Physics. *You work it out.*

[Home](#) [Gameboard](#) [Physics](#) [Electricity](#) [Resistors](#) [Potential Dividers 4](#)

# Potential Dividers 4

Essential Pre-Uni Physics C5.4

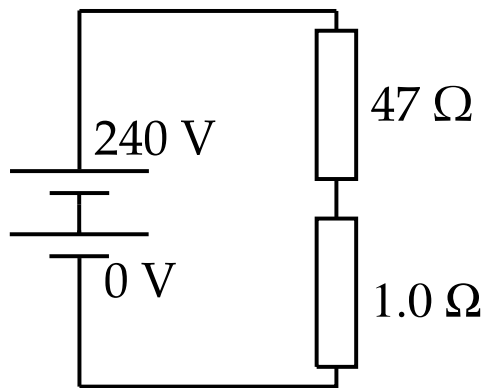

**Figure 1:** Circuit diagram

What is the voltage across the lower resistor in the circuit?

Gameboard:

**STEM SMART Physics Week 2 - Circuits**


All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.



# Potential Dividers 6

Essential Pre-Uni Physics C5.6

A Level

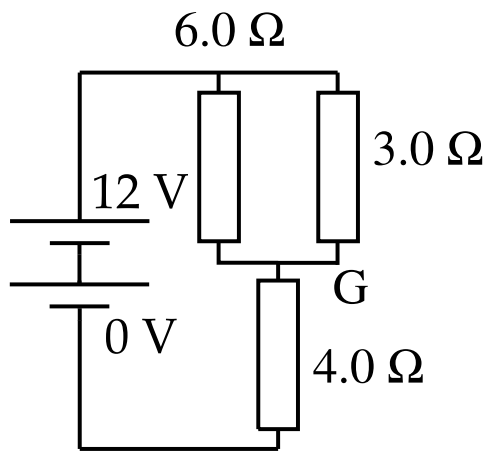

**Figure 1:** Circuit diagram

What is the potential at G, the junction between the two resistors in parallel and the one in series, in this circuit?

Gameboard:

**STEM SMART Physics Week 2 - Circuits**

All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.

# Potential Dividers 8

## Essential Pre-Uni Physics C5.8

---



A thermistor has a resistance of  $800\ \Omega$  at a temperature of  $16\ ^\circ\text{C}$ . It is wired in series with a fixed resistor and a  $9.0\ \text{V}$  battery. A high-resistance voltmeter is connected to give a 'temperature' reading.

[Note: For this thermistor the resistance decreases as the temperature increases.]

### Part A Connecting the voltmeter

---

a) If the voltage reading is to go up when the temperature increases, should the voltmeter be connected in parallel with the thermistor or the fixed resistor?

- ☐ Fixed resistor
- ☐ Thermistor

### Part B Resistance of the fixed resistor

---

b) If the voltmeter needs to read  $3.0\ \text{V}$  when the temperature is  $16\ ^\circ\text{C}$ , what is the resistance of the fixed resistor to 2 significant figures?

Gameboard:

[STEM SMART Physics Week 2 - Circuits](#)



Physics. *You work it out.*

[Home](#) [Gameboard](#) [Physics](#) [Electricity](#) [Internal Resistance](#) [Internal Resistance 4](#)

# Internal Resistance 4

A Level



## Essential Pre-Uni Physics C6.4

---

A high-resistance voltmeter is connected in parallel with a portable battery used to start cars. Before the car is connected, the meter reads  $12.4\text{ V}$ . When the car is connected, and a  $64\text{ A}$  current is flowing, the meter reads  $11.5\text{ V}$ .

### Part A E.m.f. of the battery

What is the e.m.f. of the battery to 3 significant figures?

---

### Part B Internal resistance of the battery

What is the internal resistance of the battery?

---

Gameboard:

[\*\*STEM SMART Physics Week 2 - Circuits\*\*](#)


All materials on this site are licensed under the [\*\*Creative Commons license\*\*](#), unless stated otherwise.

# Batteries and Resistors in Parallel

**GCSE**  
C C C

**A Level**  
P P P

In the circuit diagram shown below,  $R_1 = 3.0 \, \Omega$ ,  $R_2 = 2.0 \, \Omega$ ,  $R_3 = 5.0 \, \Omega$  and two ideal batteries with  $V = 1.5 \, \text{V}$ .

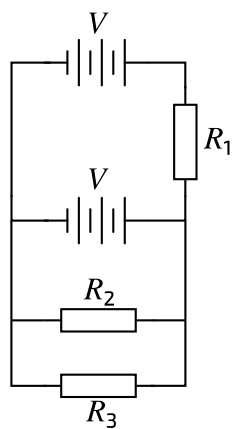

**Figure 1:** Circuit diagram showing two resistors and a battery in parallel, where the battery is also connected to a resistor and another battery in series.

## Part A Power dissipated by a resistor

What is the power dissipated by the resistor with resistance  $R_1$ ?

## Part B Power dissipated by another resistor

What is the power dissipated by the resistor  $R_3$ ?


All materials on this site are licensed under the **Creative Commons license**, unless stated otherwise.



# A Power Problem

GCSE A Level  
C C C C C C

The circuit shown in the figure below is made up of a battery connected to a set of resistors with different values of resistance. However, if a power of over  $2.00 \text{ W}$  is dissipated in one of these resistors, that resistor will fail.

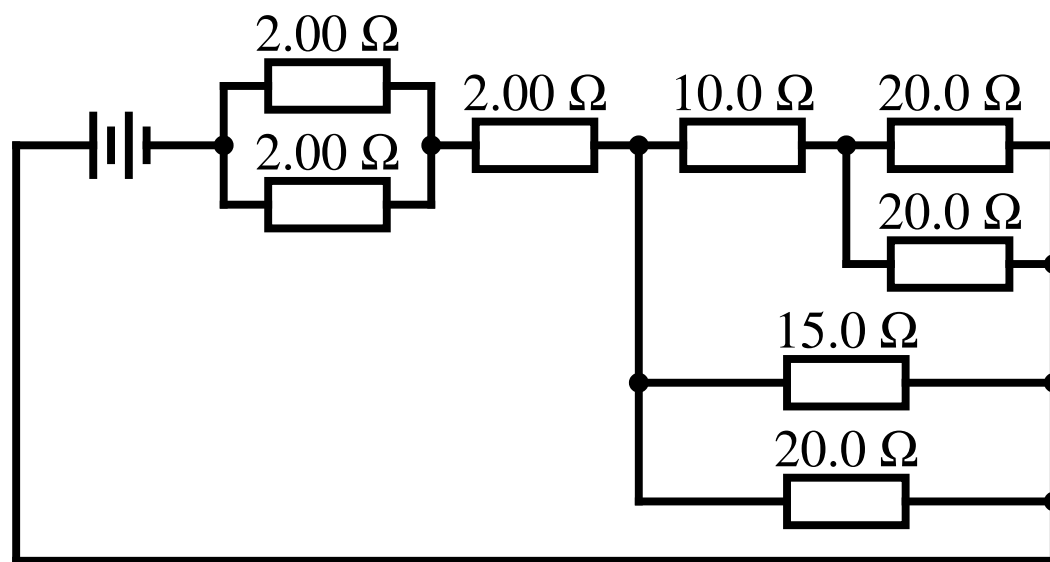

**Figure 1:** Circuit diagram showing a resistor network with the resistance values on the resistors.

What is the maximum voltage of the battery that can be used without any of the resistors failing?