

I2 Capacitor Networks

- I2.1 Calculate the capacitance of each of the following combinations:
- a) A $3.0\ \mu\text{F}$ capacitor connected in parallel with a $2.0\ \mu\text{F}$ capacitor.
 - b) A $3.0\ \mu\text{F}$ capacitor connected in series with a $2.0\ \mu\text{F}$ capacitor.
 - c) A $6.0\ \mu\text{F}$ capacitor is connected in parallel with a $4.0\ \mu\text{F}$ capacitor. The combination is then connected in series with a $20\ \mu\text{F}$ capacitor.
 - d) A $220\ \text{nF}$ capacitor is connected in series with a $440\ \text{nF}$ capacitor. The combination is connected in parallel with a $1.0\ \mu\text{F}$ capacitor.
 - e) A $1.0\ \text{nF}$, $2.0\ \text{nF}$ and $3.0\ \text{nF}$ capacitor, all connected in parallel.
 - f) A $1.0\ \text{nF}$, $2.0\ \text{nF}$ and $3.0\ \text{nF}$ capacitor, all connected in series.
- I2.2 A $200\ \mu\text{F}$ capacitor is in series with a $2200\ \mu\text{F}$ capacitor and they are charged until the $200\ \mu\text{F}$ capacitor stores $30\ \mu\text{C}$. What is the charge on the other capacitor?
- I2.3 A $200\ \mu\text{F}$ capacitor is in series with a $2200\ \mu\text{F}$ capacitor. The capacitors are charged until the $200\ \mu\text{F}$ capacitance has a voltage of $12\ \text{V}$ across it. What is the voltage across the $2200\ \mu\text{F}$ capacitor?
- I2.4 A $470\ \mu\text{F}$ capacitor is charged using a $10\ \text{V}$ battery. It is then disconnected from the battery, and connected to an uncharged $220\ \mu\text{F}$ capacitor. Calculate the voltage across the capacitors once the current has stopped flowing. (Hint: capacitors are effectively in parallel, and total charge has not changed.)
- I2.5 A $6.0\ \text{nF}$ capacitor is in parallel with a $10\ \text{nF}$ capacitor. The voltage across the $6.0\ \text{nF}$ capacitor is $36\ \text{V}$. What is the voltage across the other capacitor?