

C6 Internal Resistance

- C6.1 A battery with an e.m.f. of 12.0 V is supplying 50 A at 10.5 V to a motor. Calculate the internal resistance of the battery.
- C6.2 A power station generator with an e.m.f. of 22 kV has an internal resistance of $0.90\text{ m}\Omega$. The current is 22 kA. Calculate the difference between the e.m.f. and the terminal p.d.
- C6.3 According to its data sheet, a portable solar cell for camping has an 'open circuit voltage' of 25.6 V. This means that the terminal p.d. is 25.6 V when no load is connected. It also has a 'short circuit current' of 2.06 A. This means that if the terminals are connected together directly a current of 2.06 A flows.
- a) State the e.m.f. of the solar cell.
 - b) Calculate the internal resistance of the solar cell.

Warning: never measure the short circuit current of a supply component unless you have been assured by a qualified professional that it is safe to do so, and that you have the correct equipment.

CHAPTER C. ELECTRIC CIRCUITS

Answers

C6.1 $\frac{12 - 10.5}{50} = 0.030 \, \Omega$

C6.2 $22 \times 10^3 \times 0.9 \times 10^{-3} = 19.8 \, \text{V}$

C6.3

a) $25.6 \, \text{V}$

b) $\frac{25.6}{2.06} = 12.427 \, \Omega$