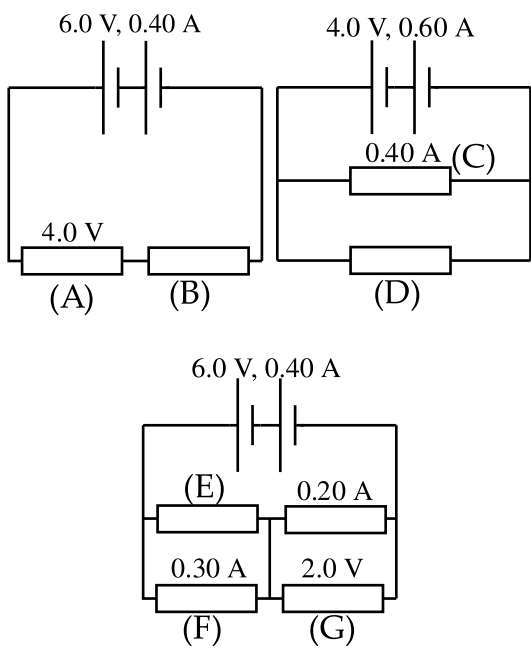


C4 Kirchhoff's Laws



Complete the table with the missing currents and potential differences.

	Resistor	Current /A	Potential difference /V
C4.1	A	(a)	2.0
	B	(b)	(c)
C4.2	C	0.4	(a)
	D	(b)	(c)
C4.3	E	(a)	(b)
	F	0.30	(c)
	G	(d)	2.0

CHAPTER C. ELECTRIC CIRCUITS

Answers

	Resistor	Current /A	Potential difference /V
C4.1	A	0.4	2.0
	B	0.4	2.0
C4.2	C	0.4	4.0
	D	0.2	4.0
C4.3	E	0.10	4.0
	F	0.30	4.0
	G	0.20	2.0